

Date:


EXPERIMENT NO. 4




AIM: Implement arithmetic and logic unit circuits in Logisim.


OBJECTIVES:


- i. Implement 1-bit, 2-bit, 4-bit and 8-bit arithmetic unit circuits**
- ii. Implement 1-bit, 2-bit, 4-bit and 8-bit logical unit circuits for four logical functions**
- iii. Implement 1-bit and 2-bit logical unit circuits for sixteen logical functions**
- iv. Implement 2-bit, 4-bit and 8-bit bidirectional shifter**
- v. Implement 1-bit, 2-bit, 4-bit and 8-bit ALU**



CIRCUITS:

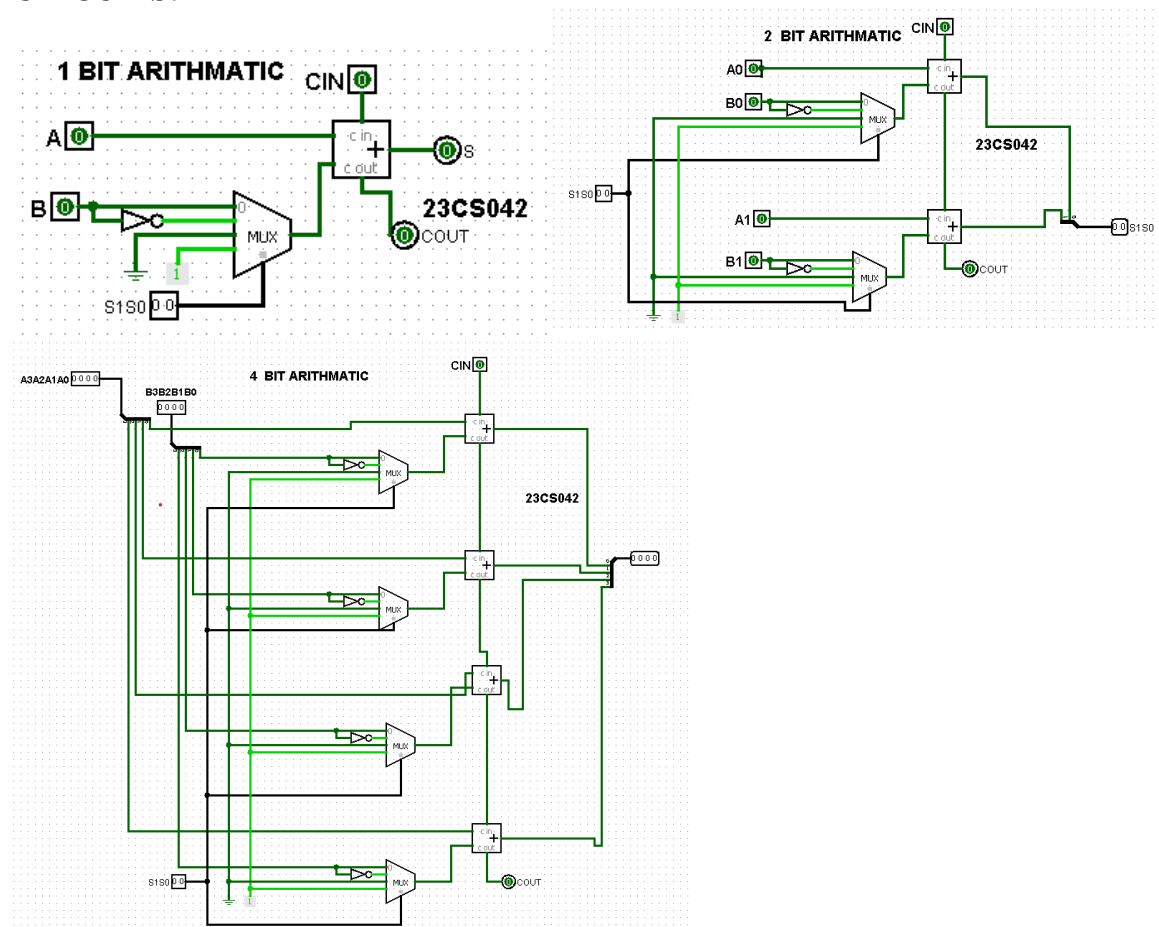


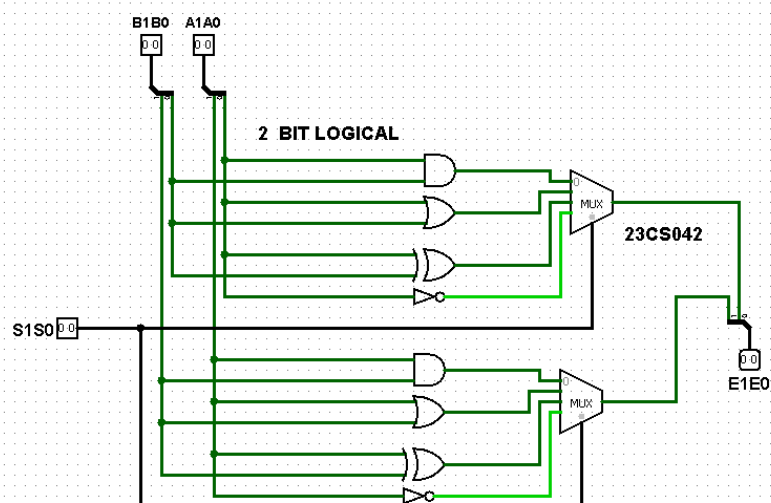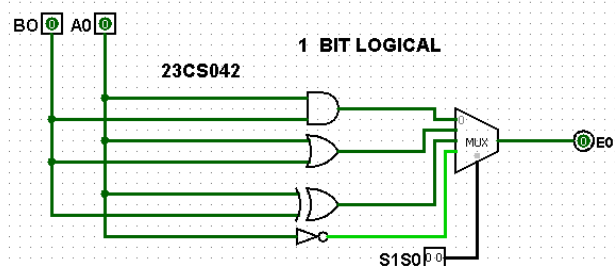
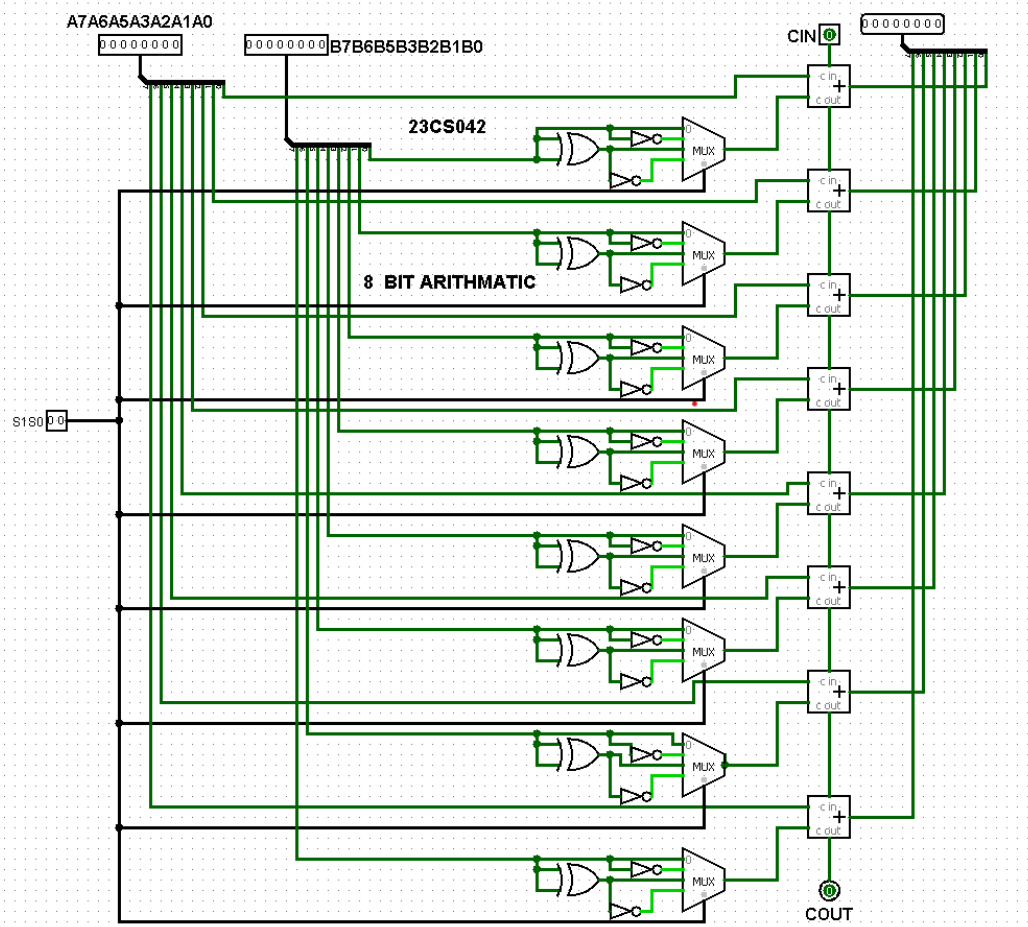


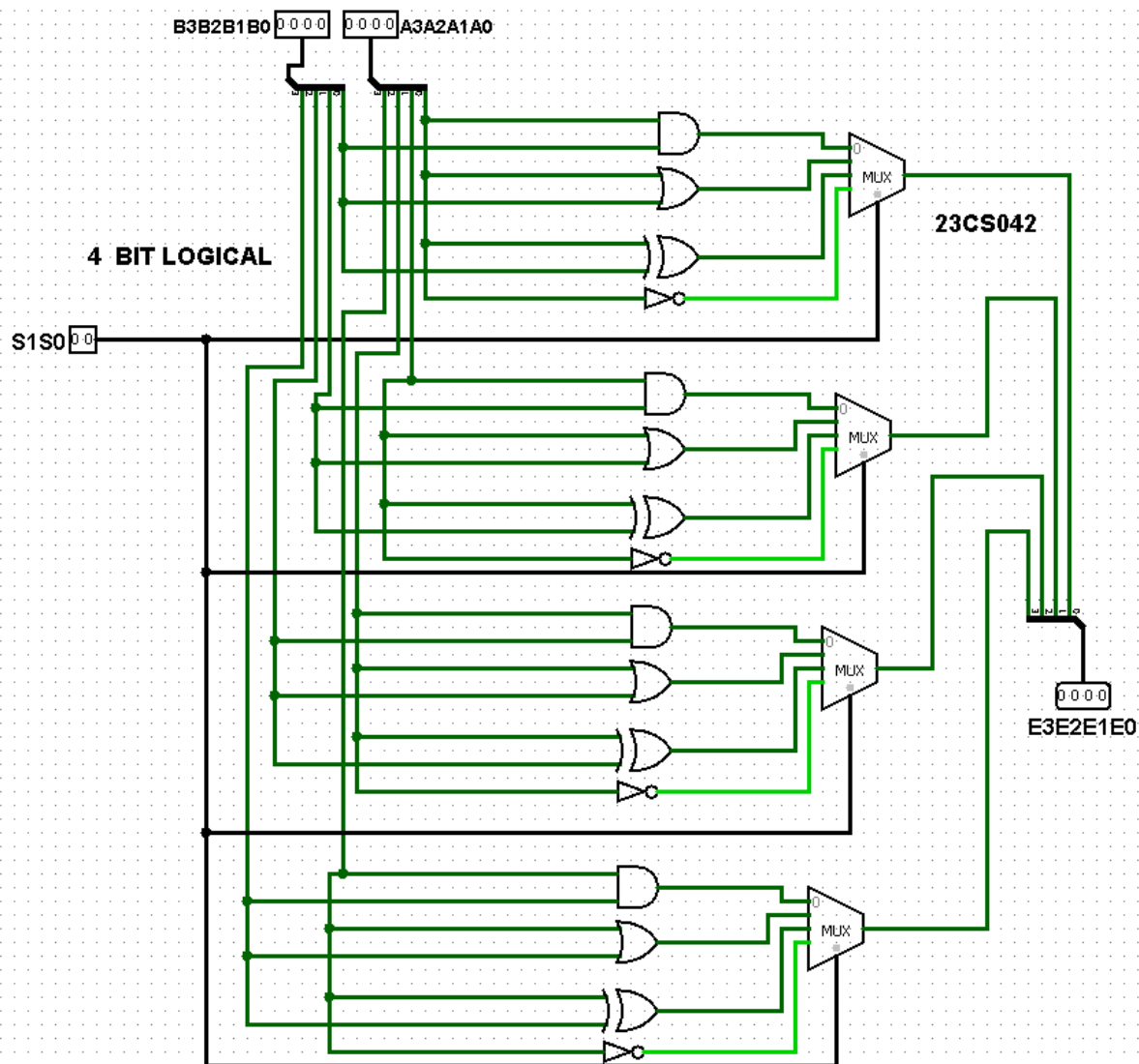


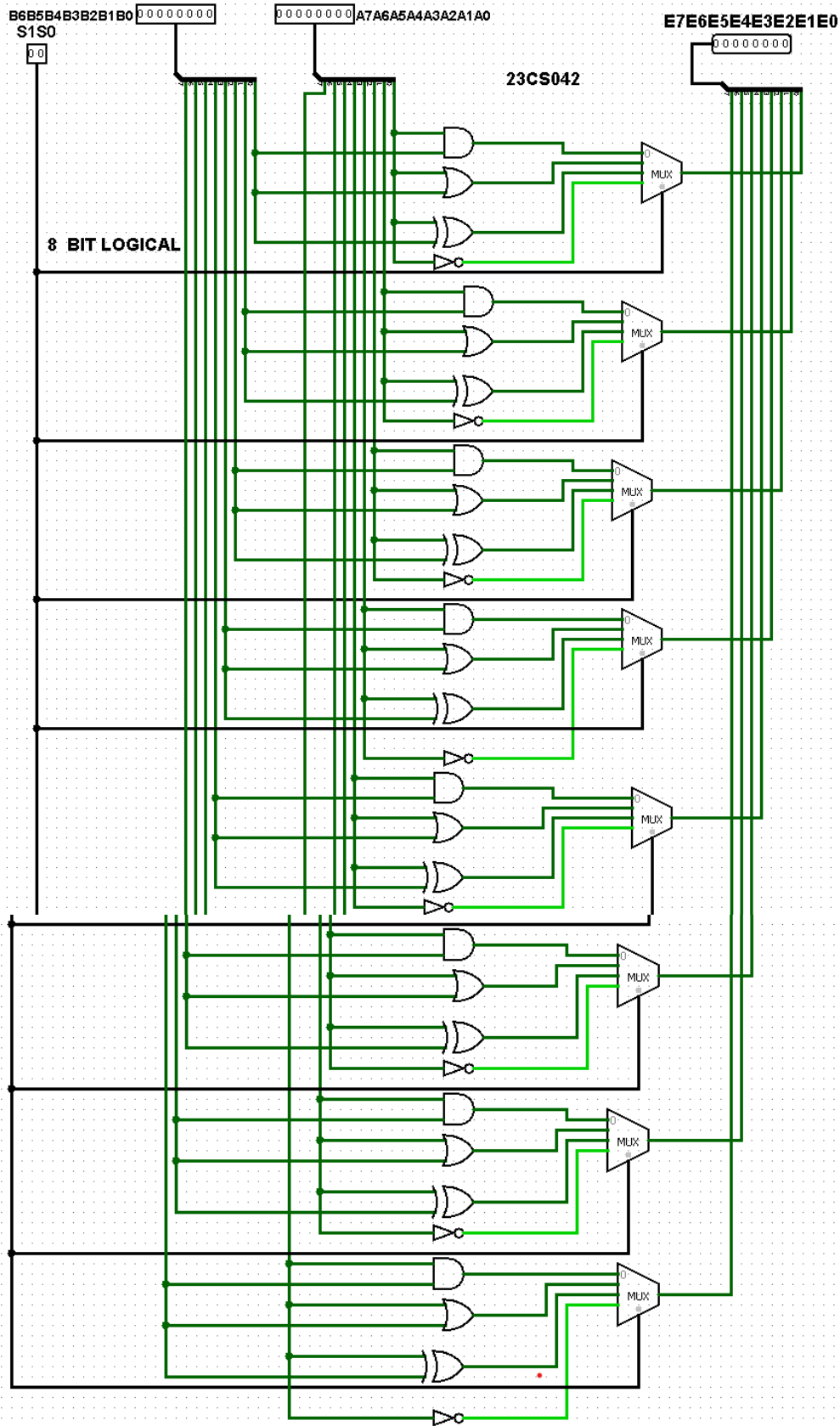

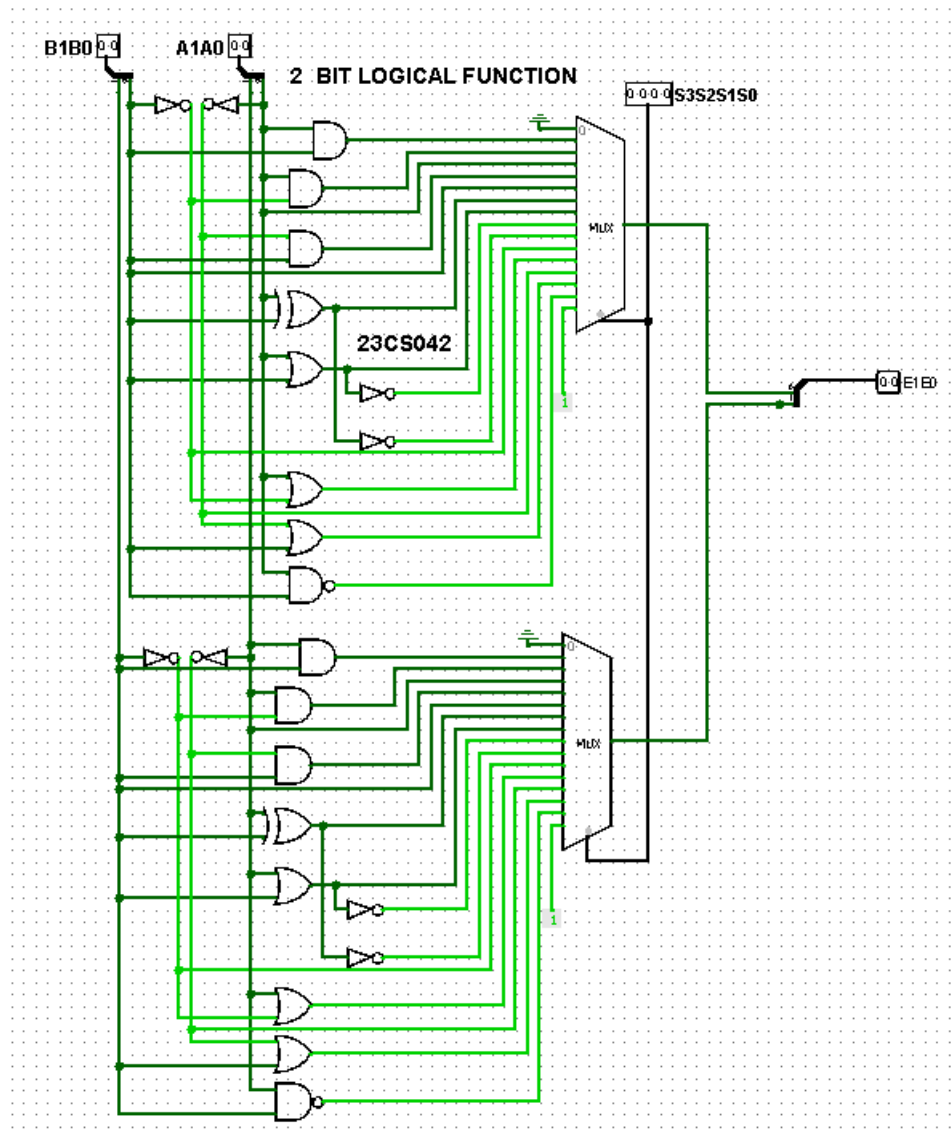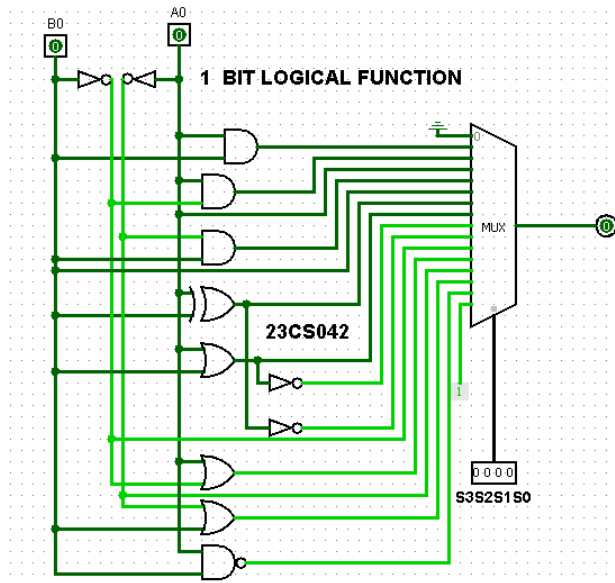




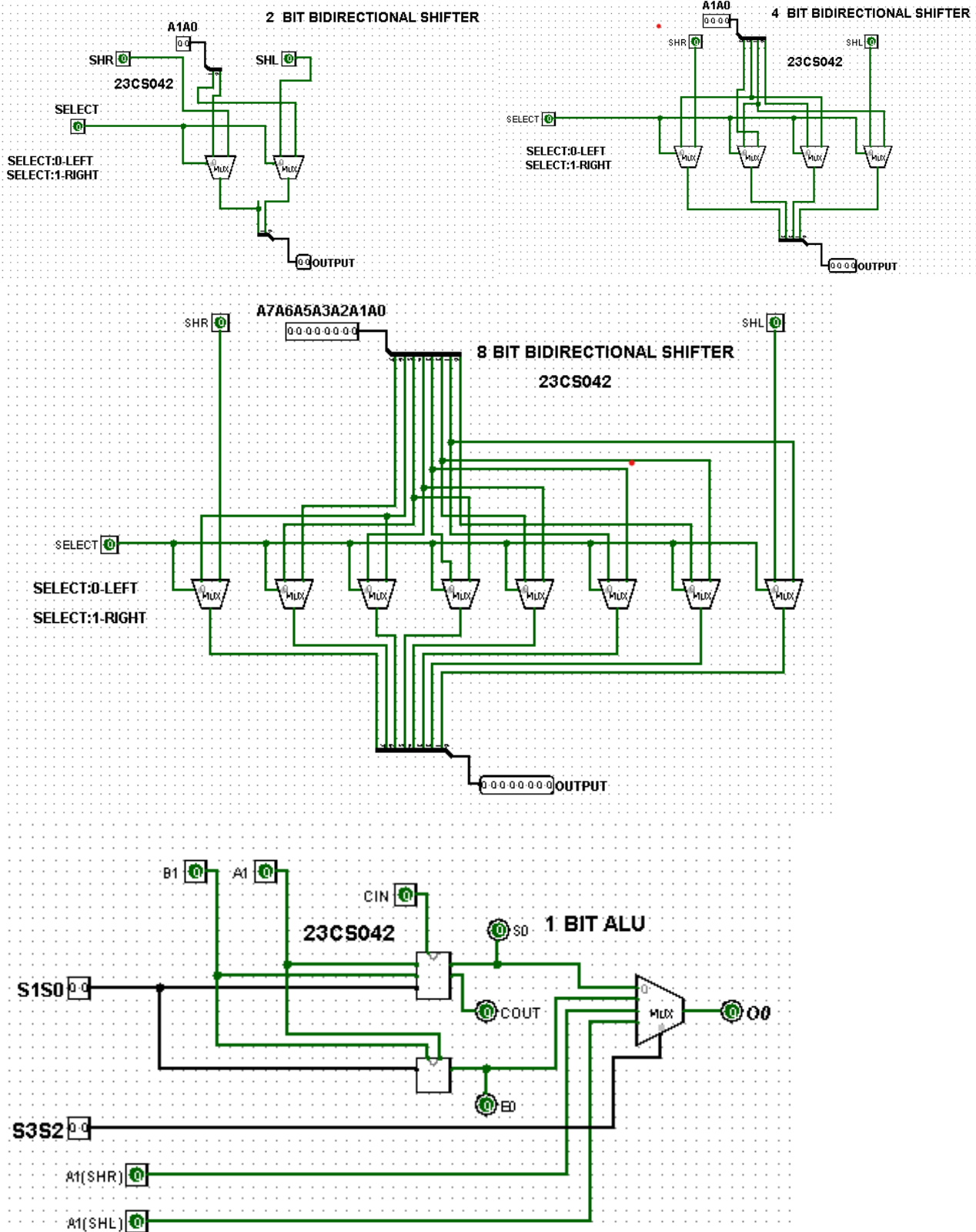



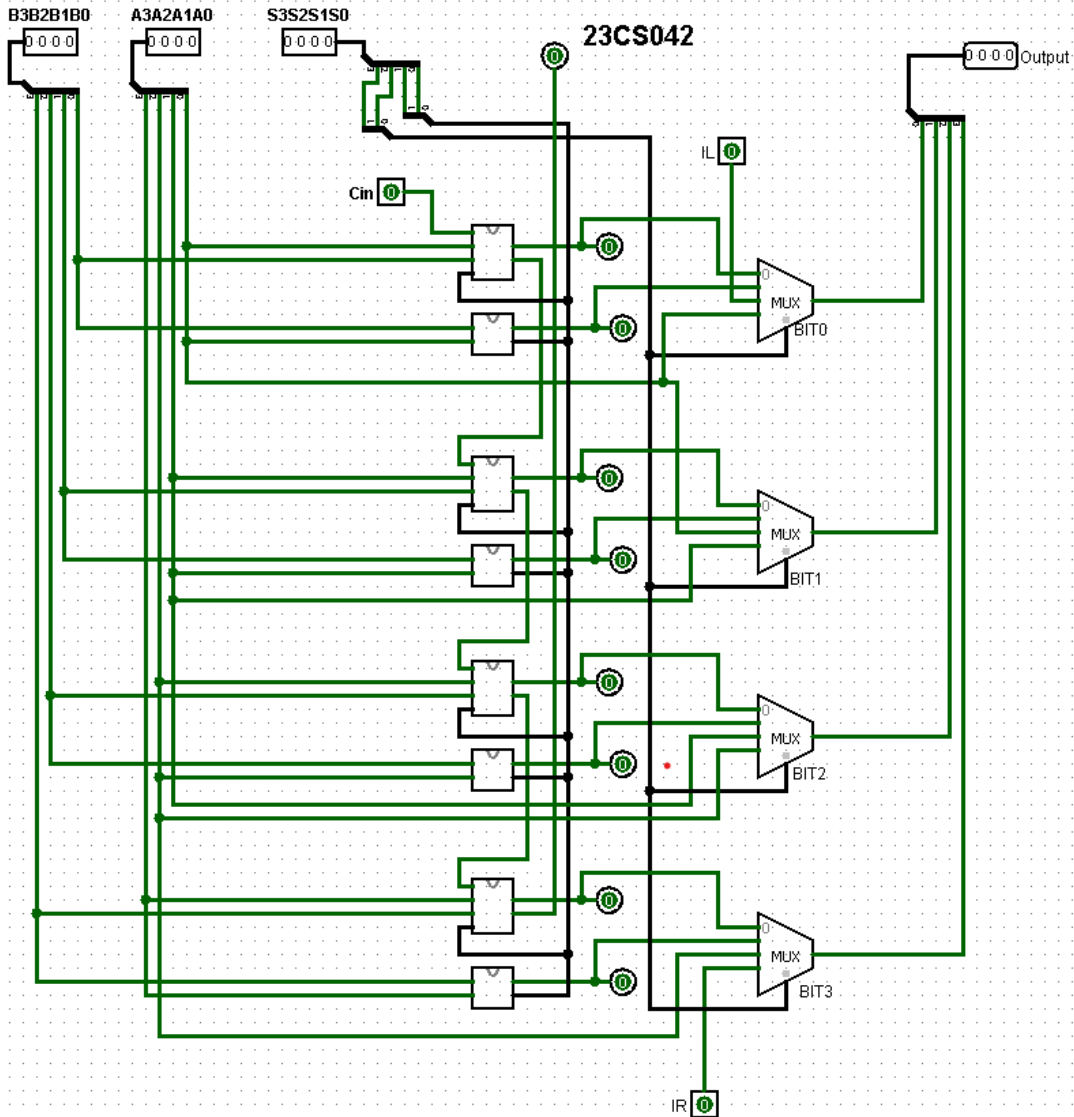
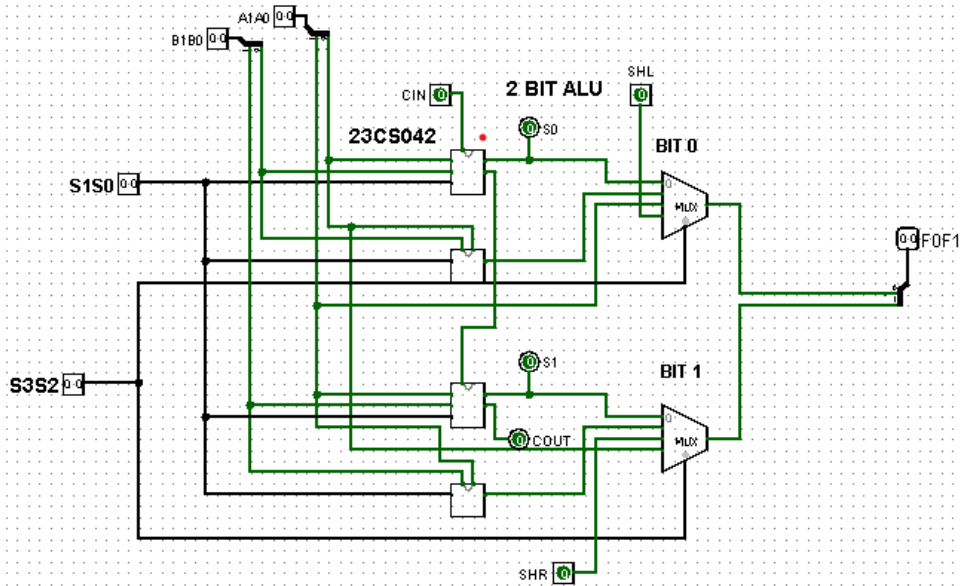




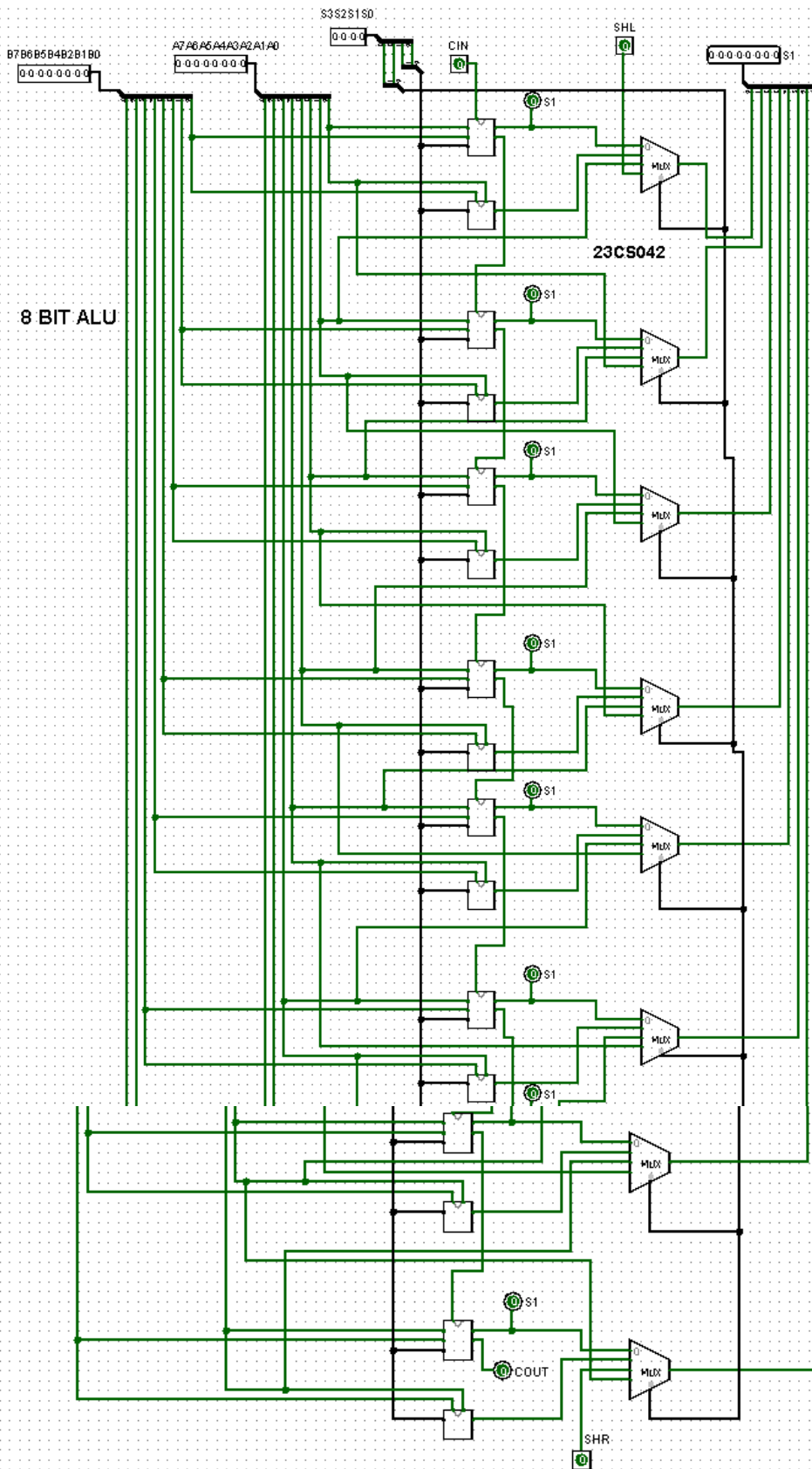



OUTPUTS:

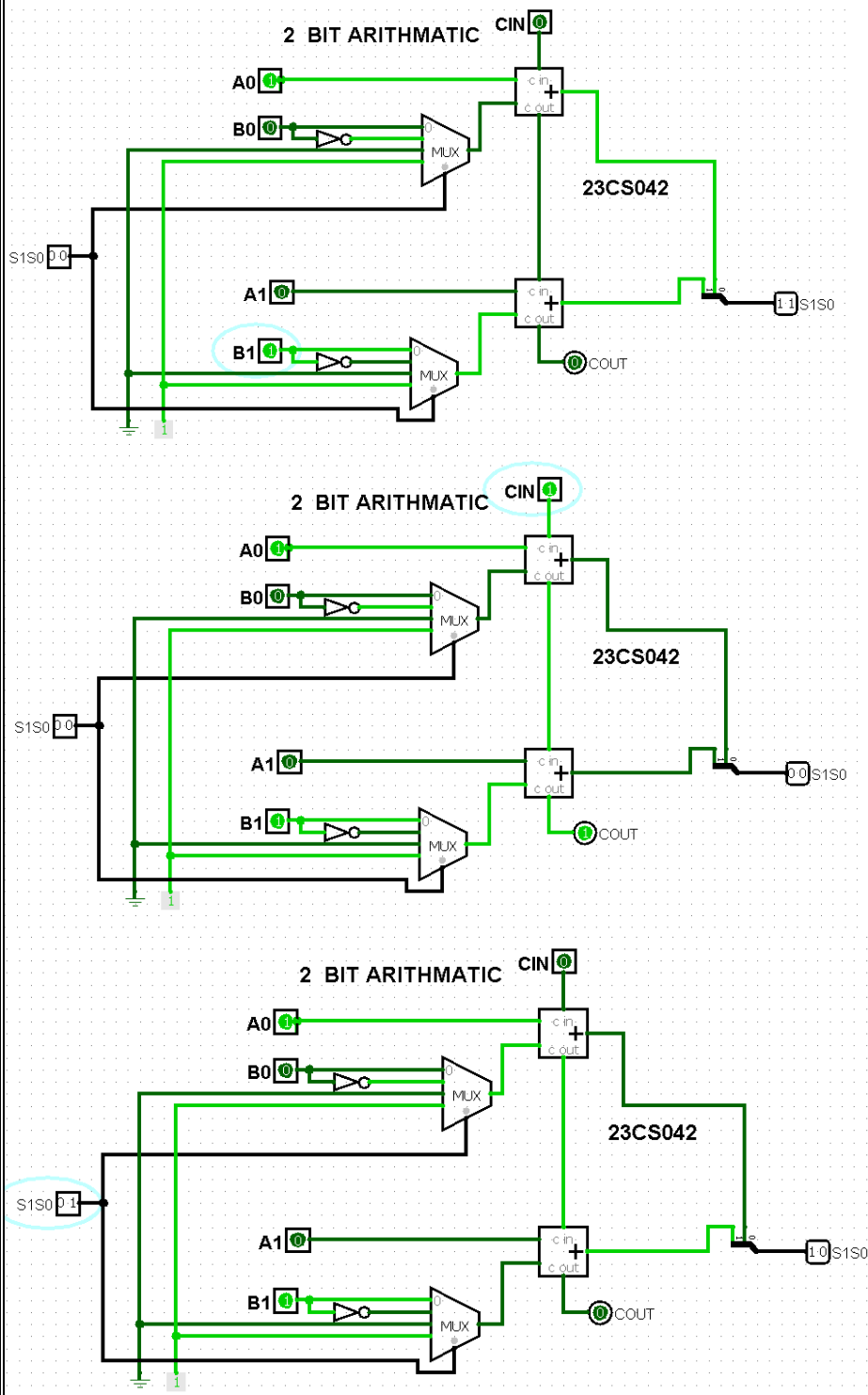


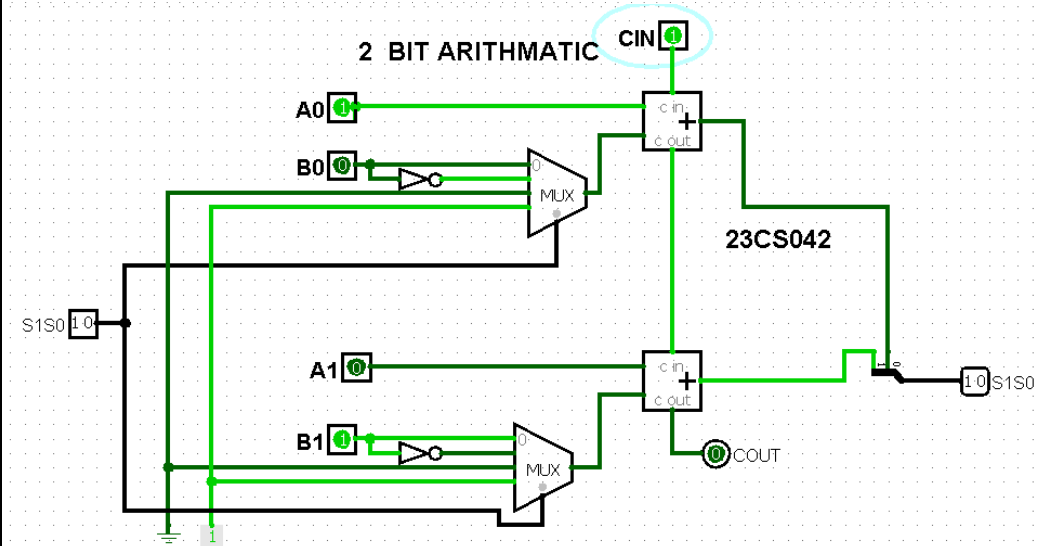
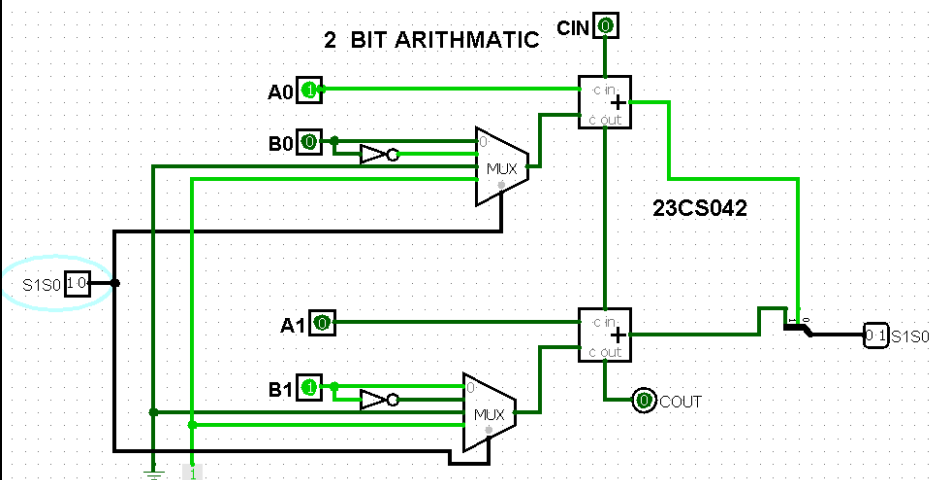
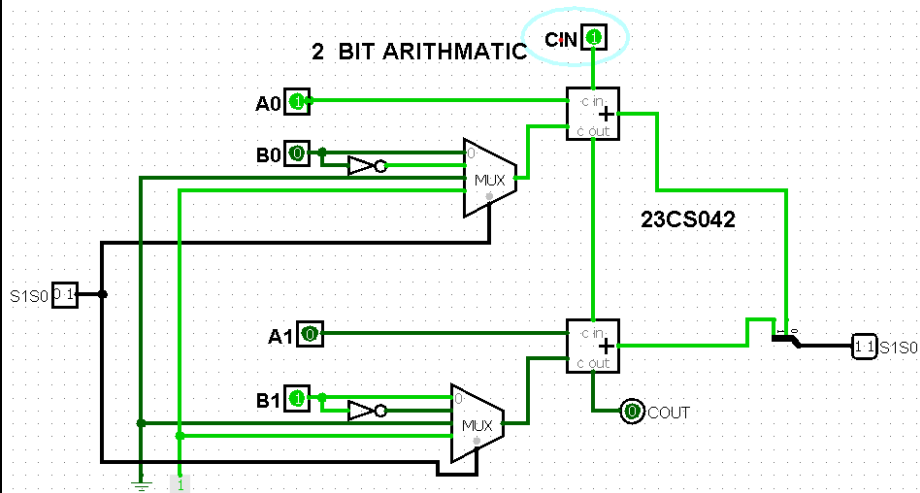


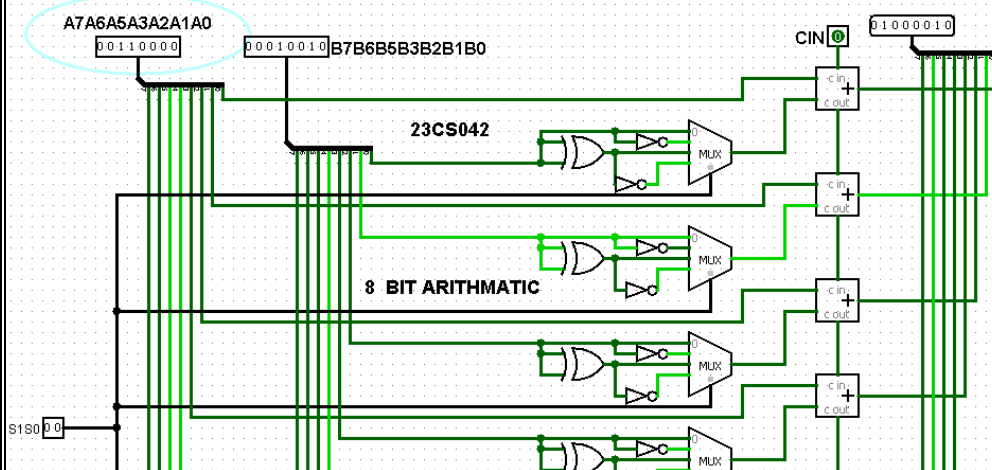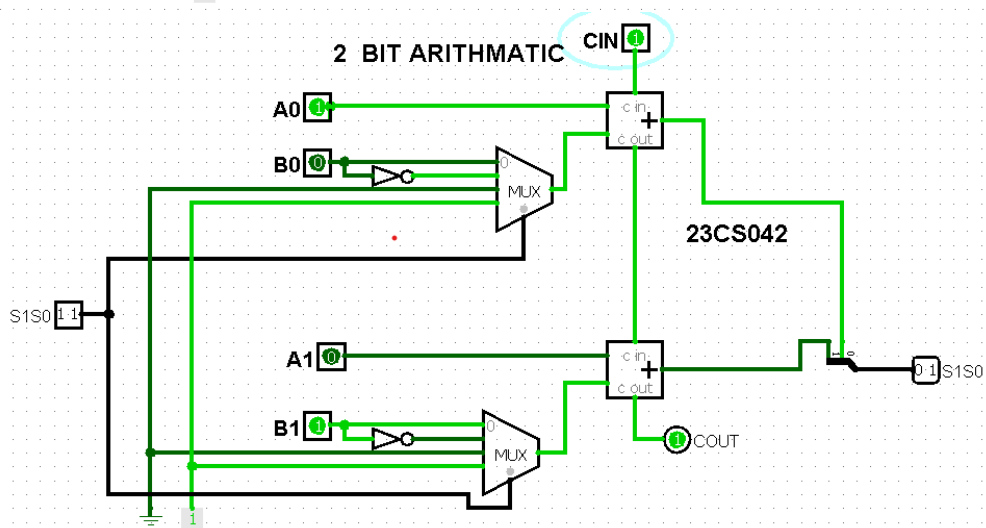
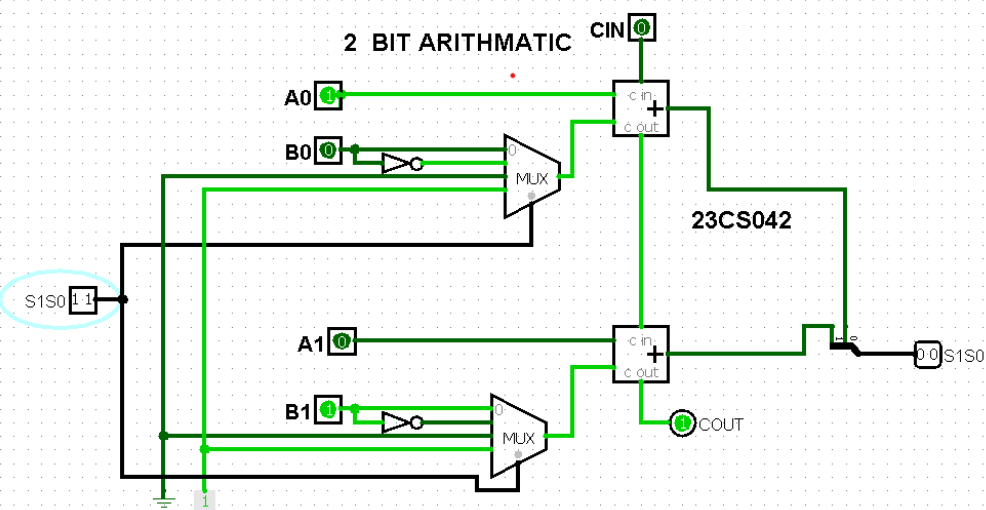


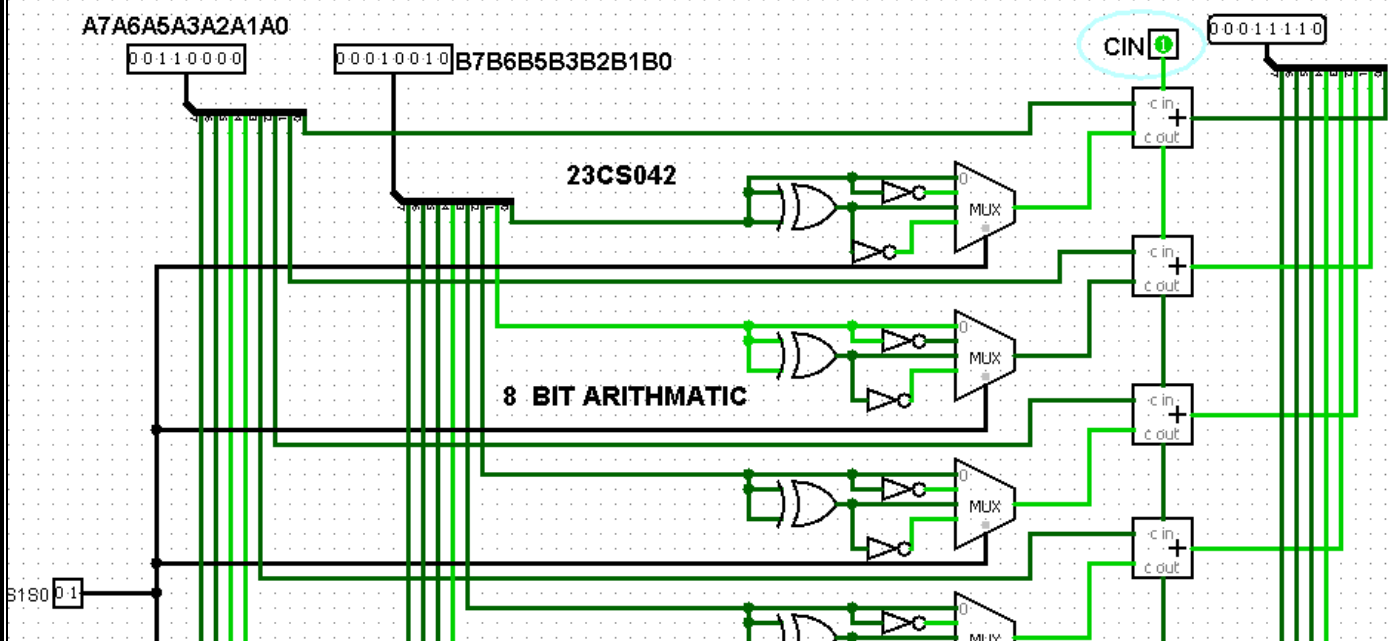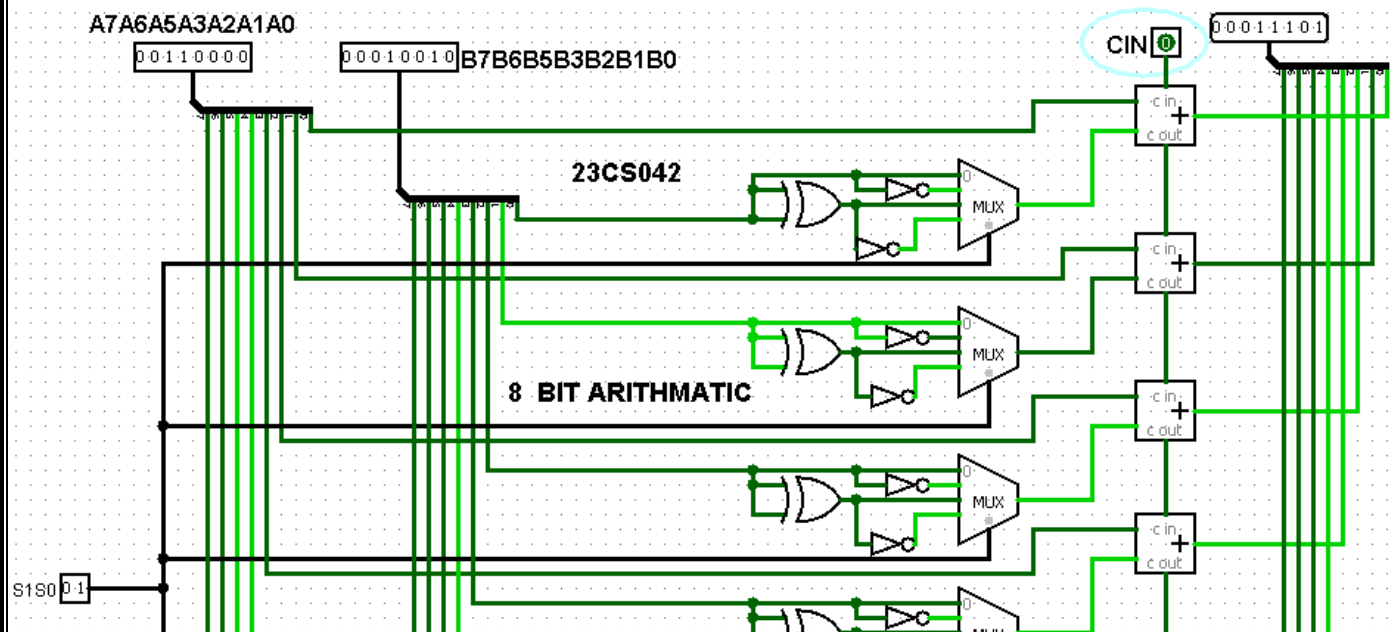
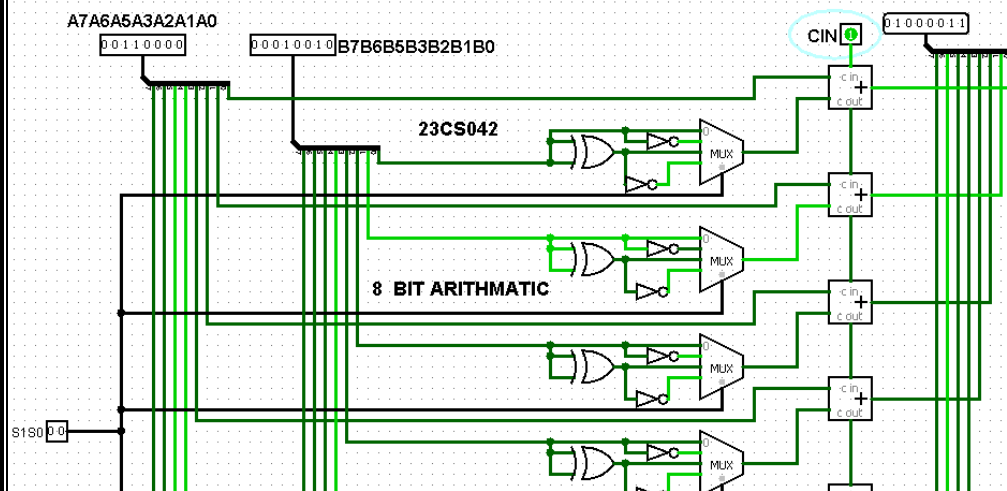





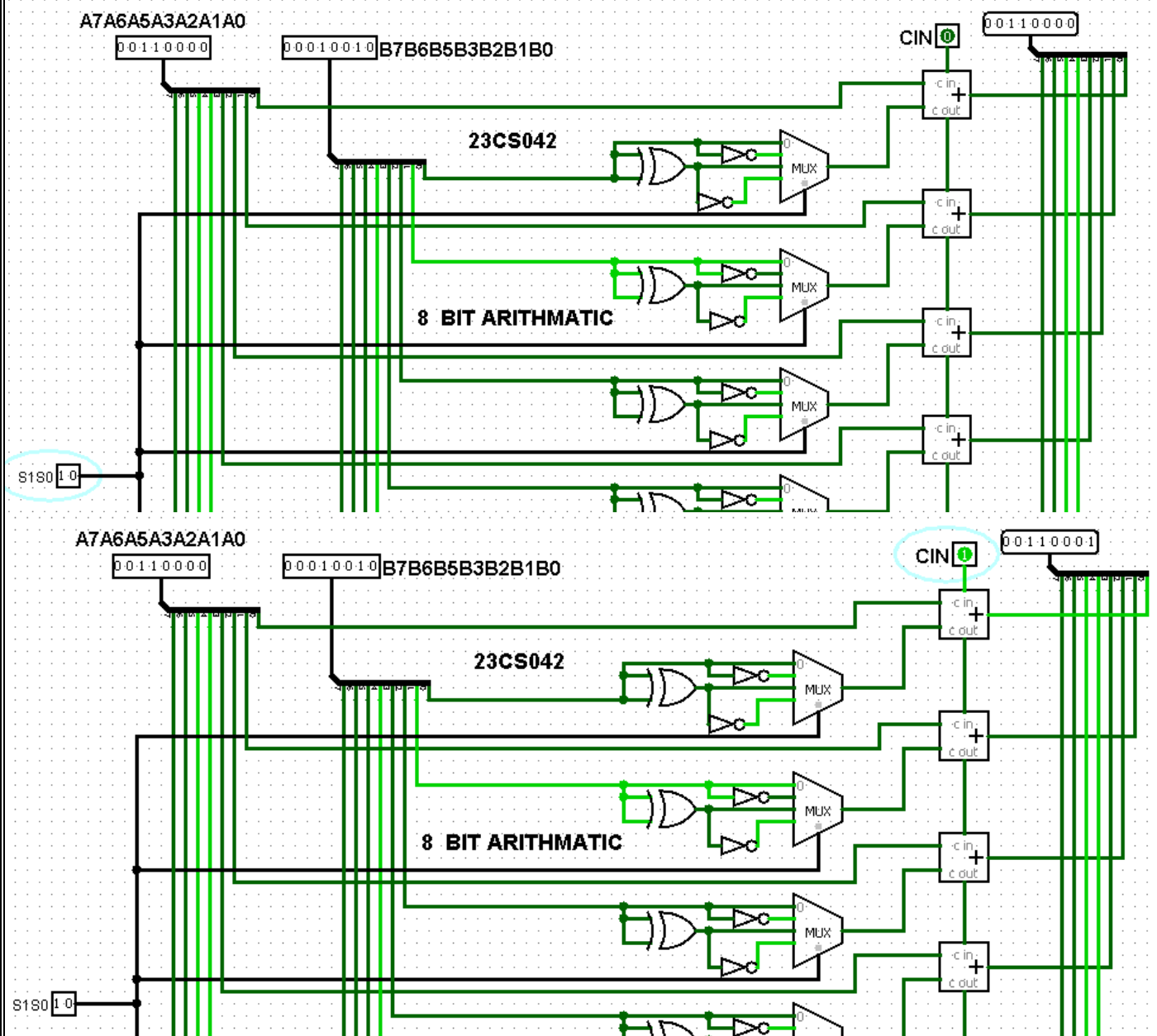





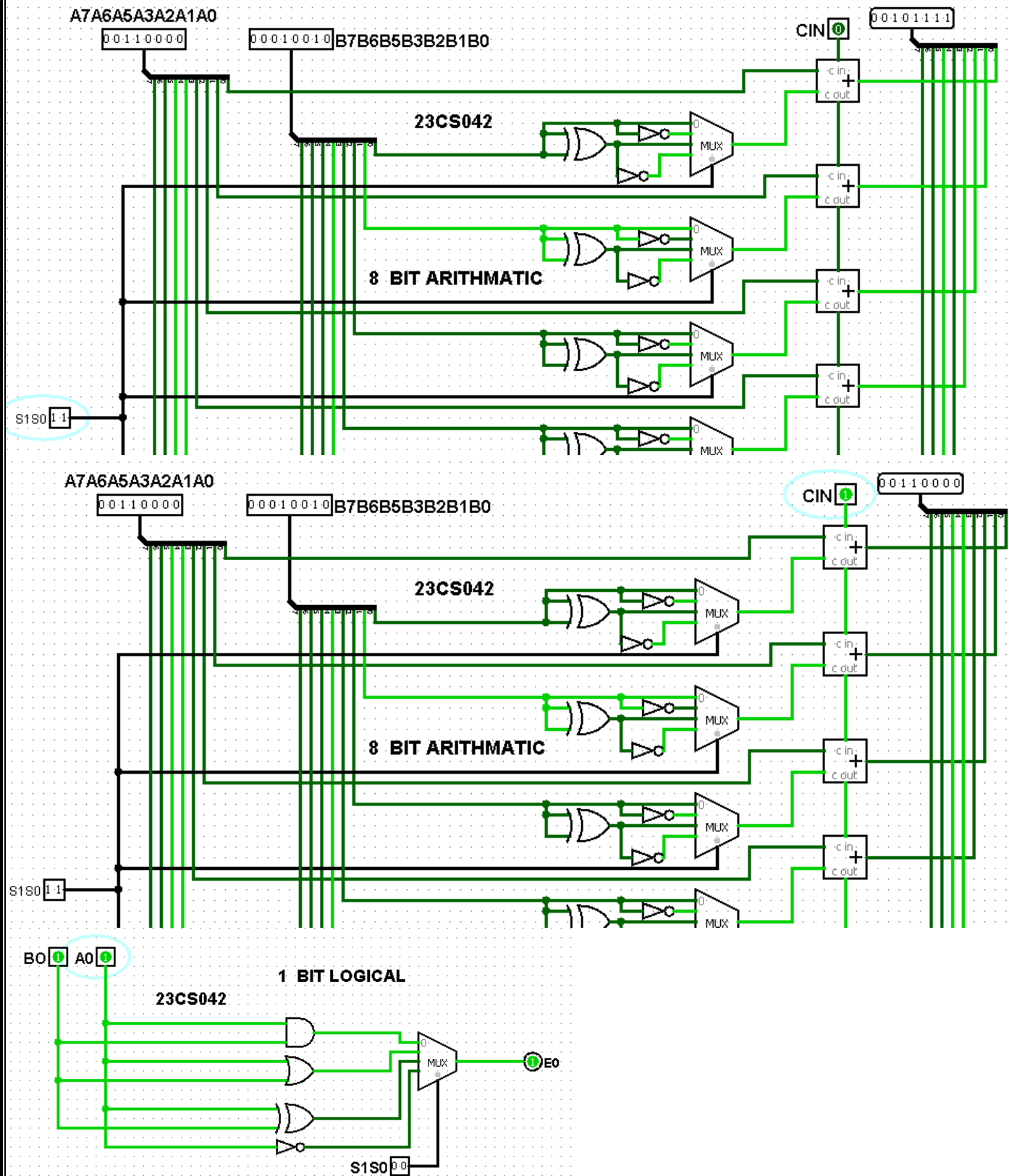


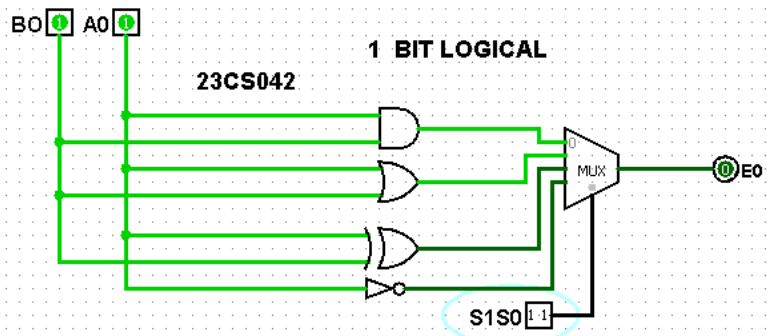
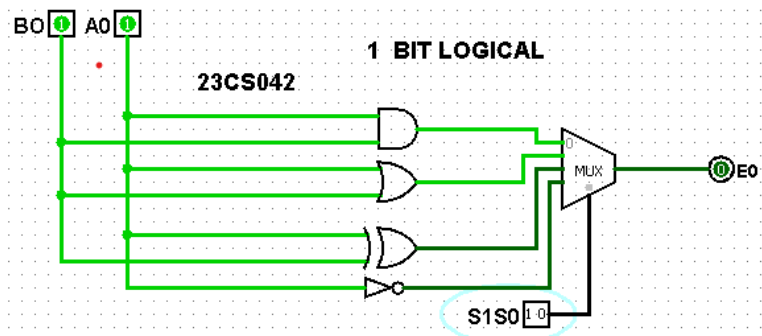
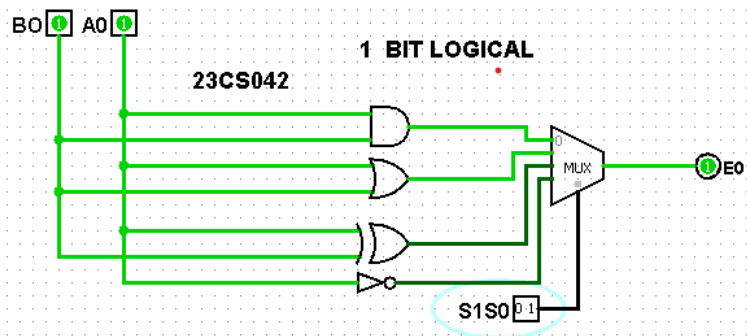




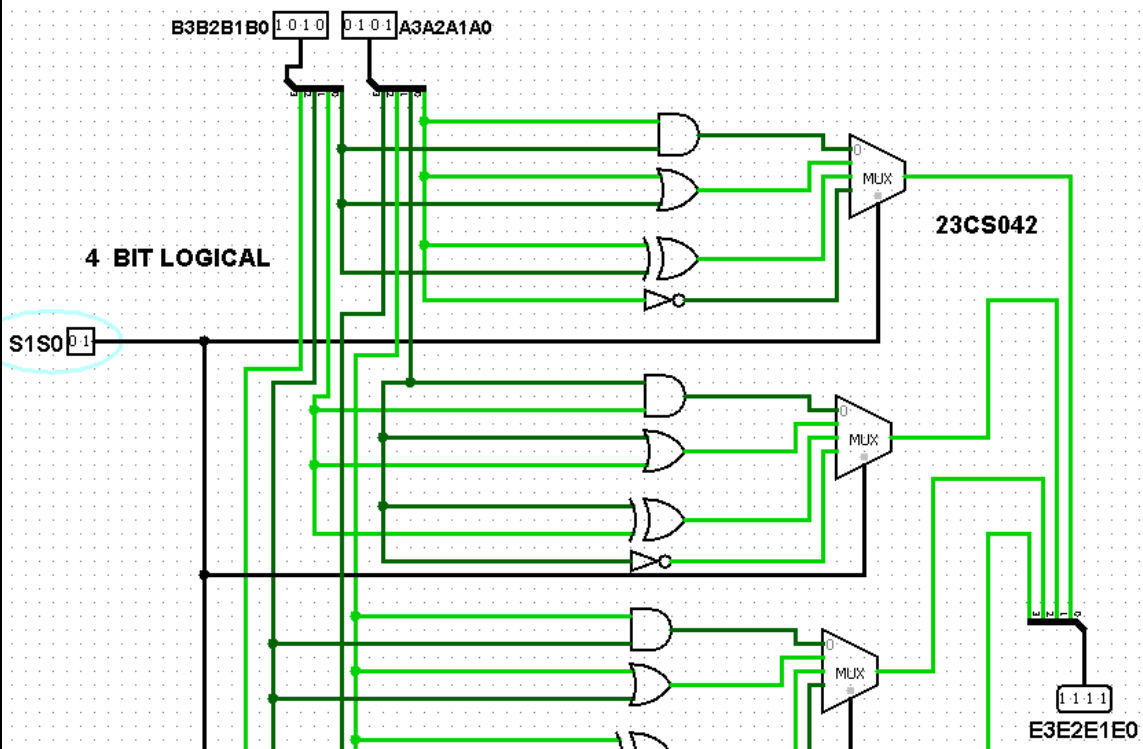
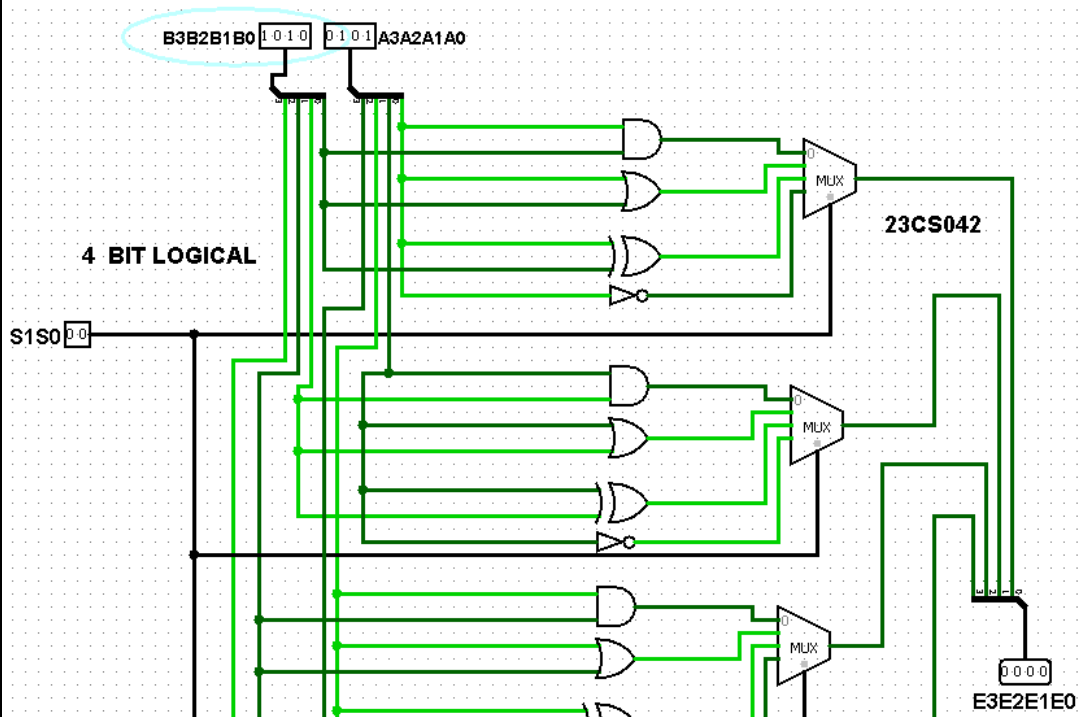



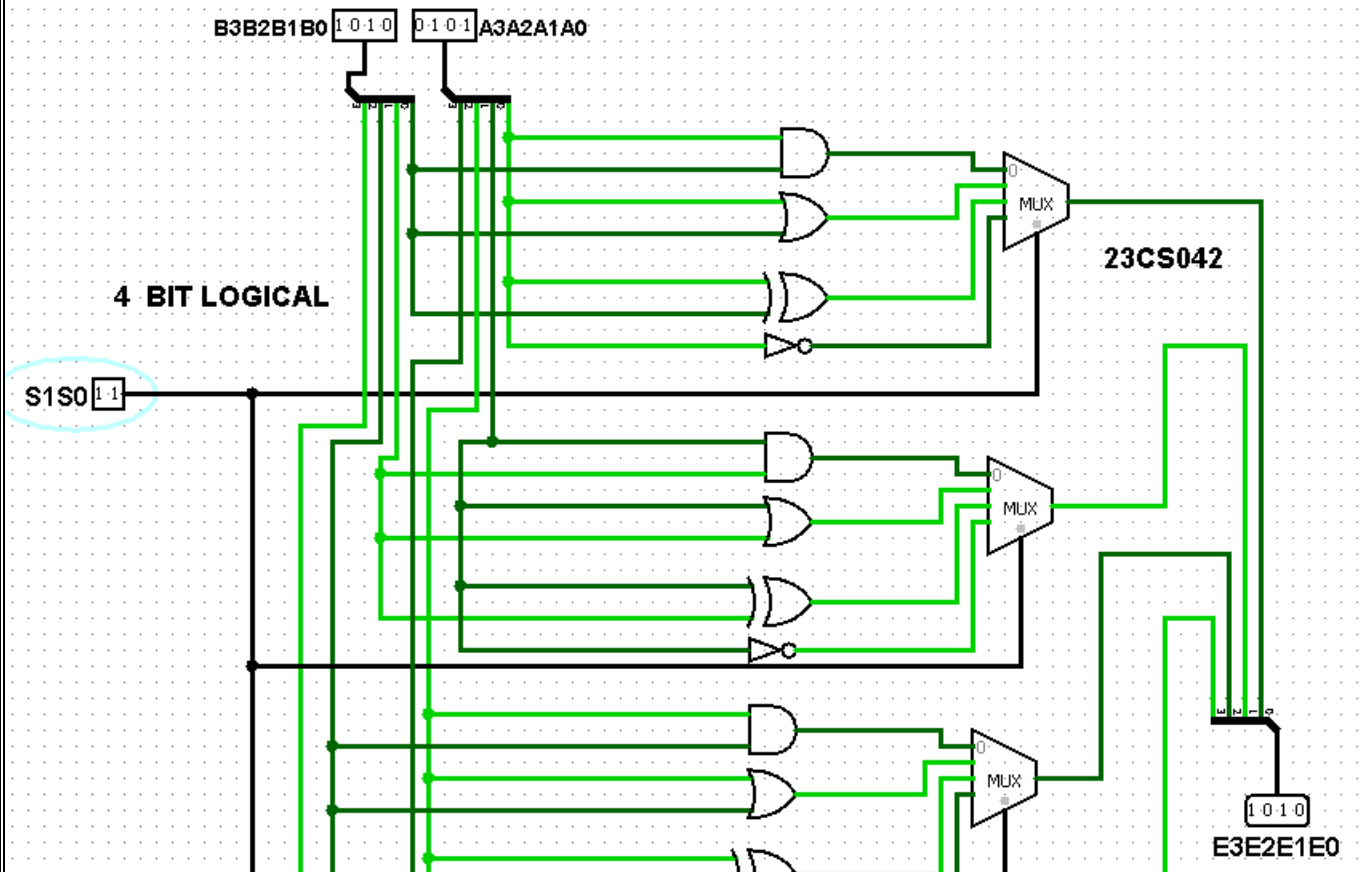
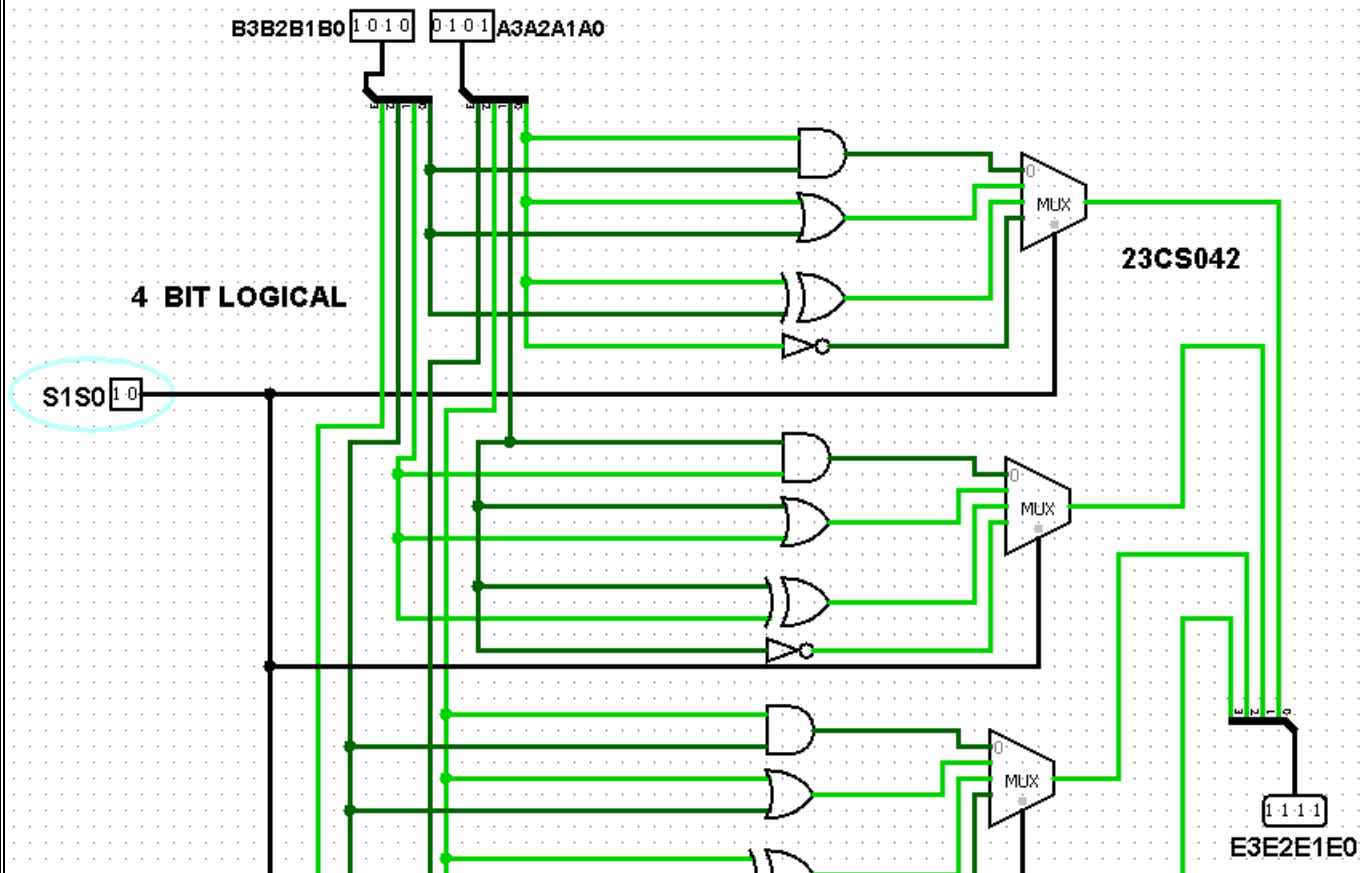


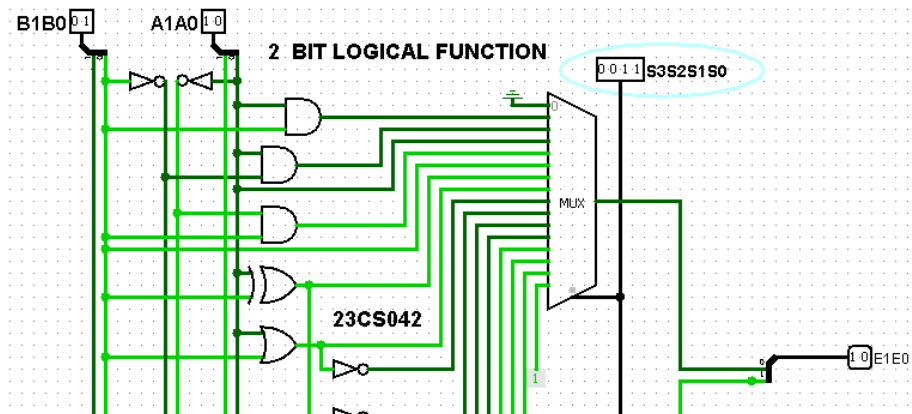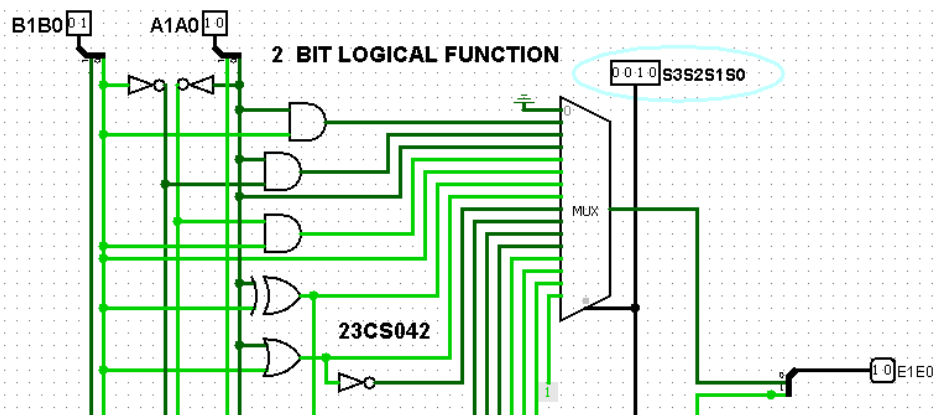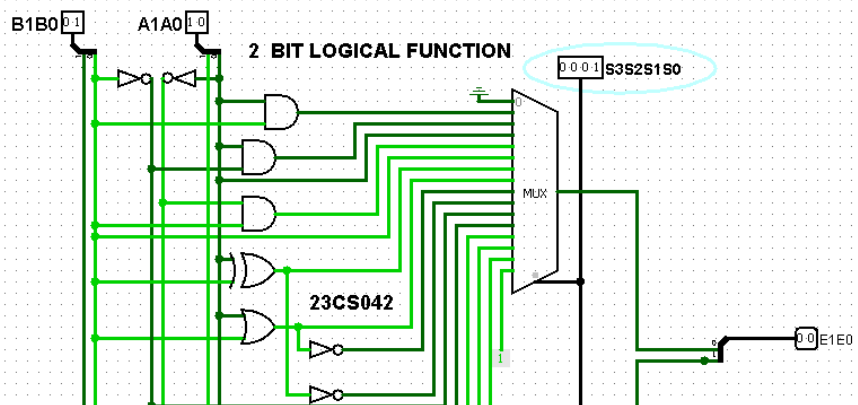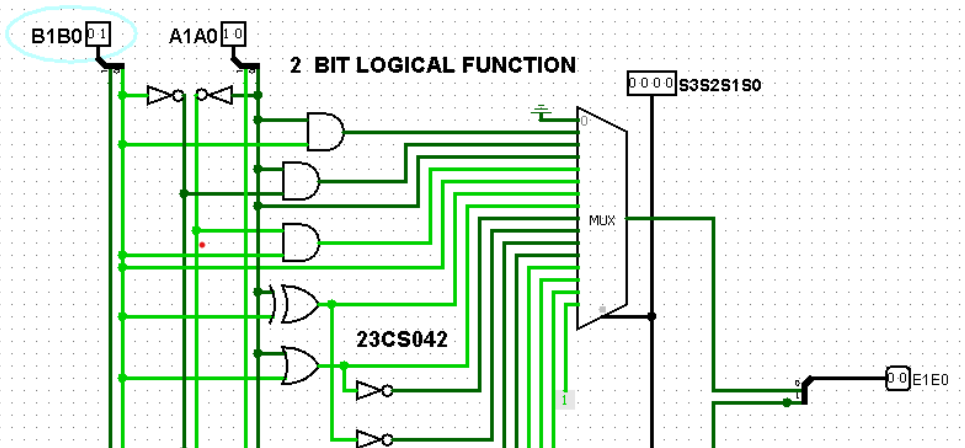

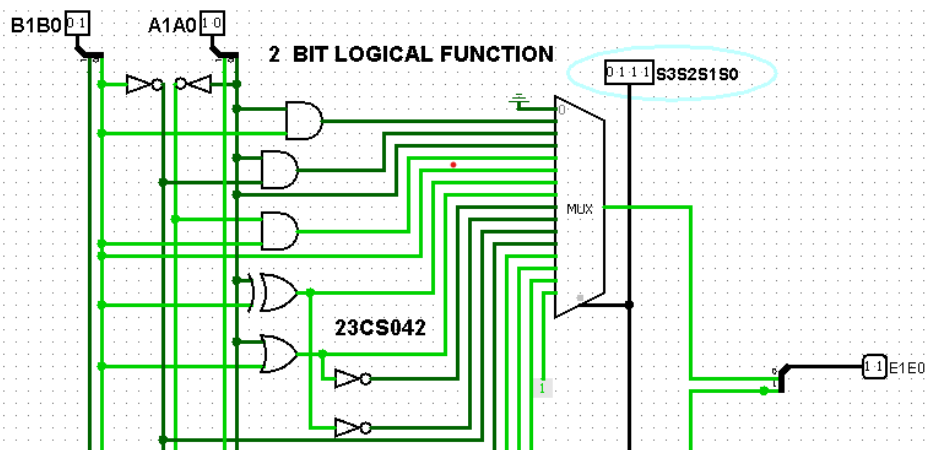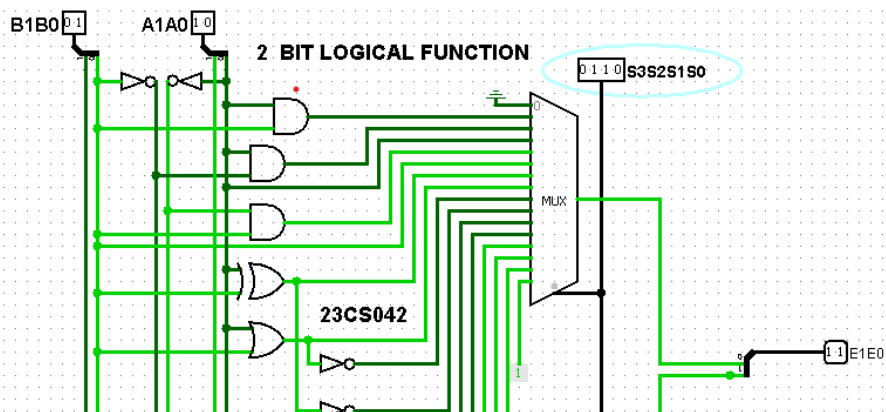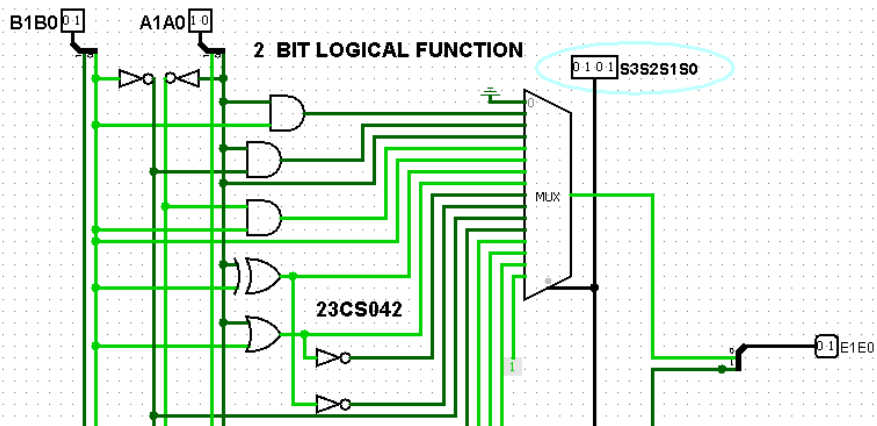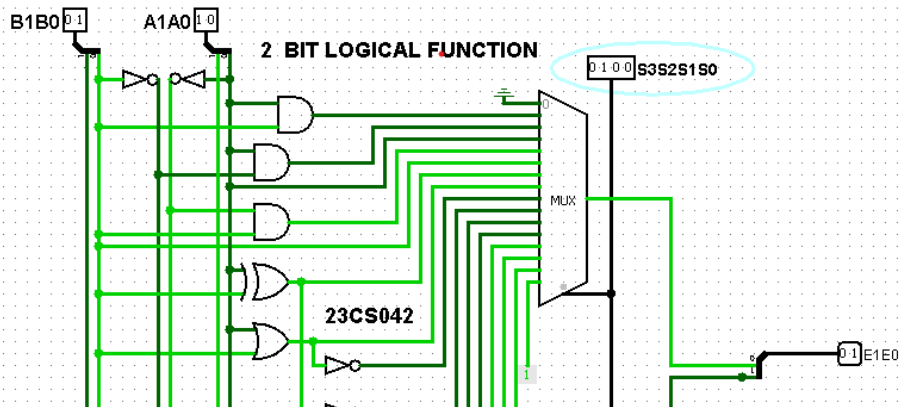


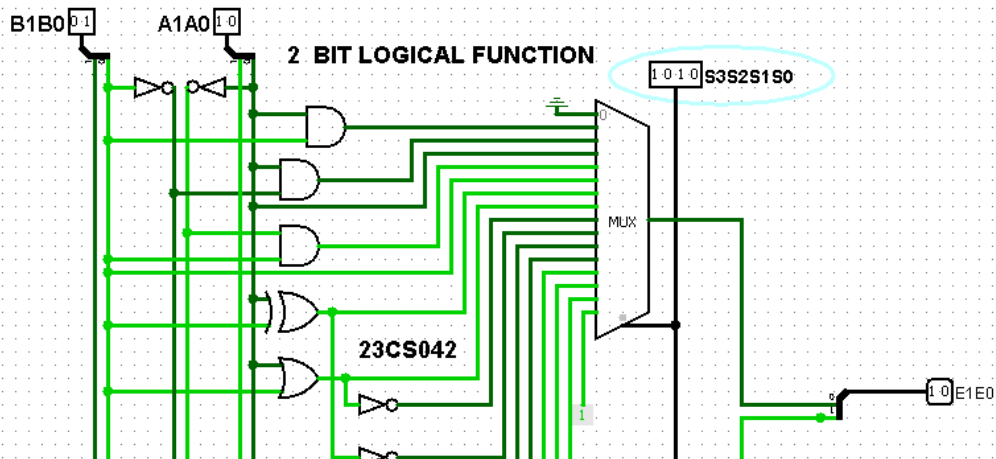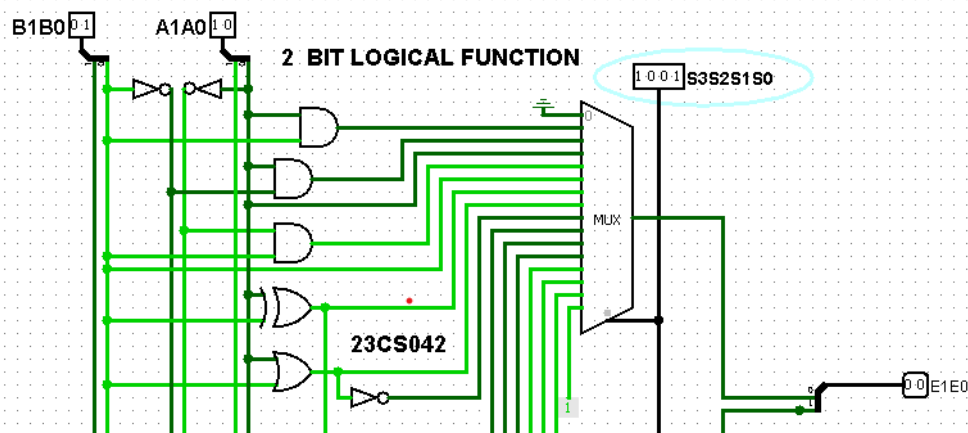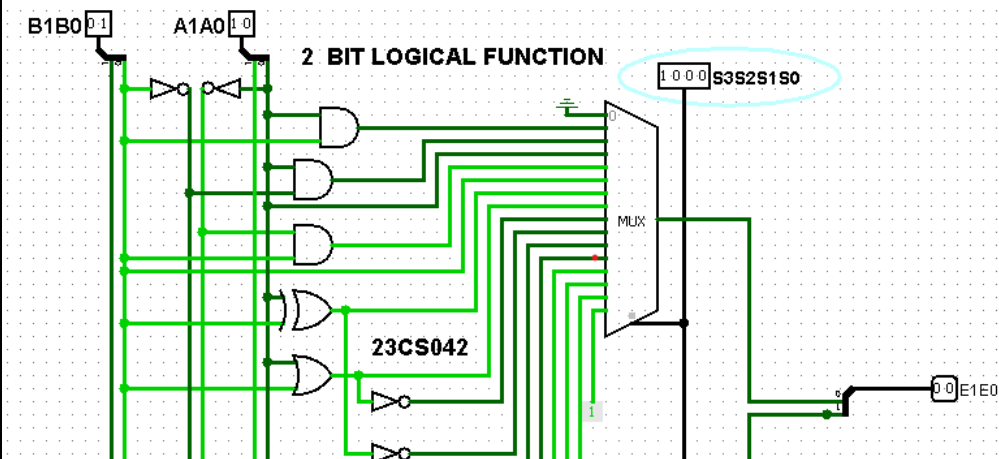

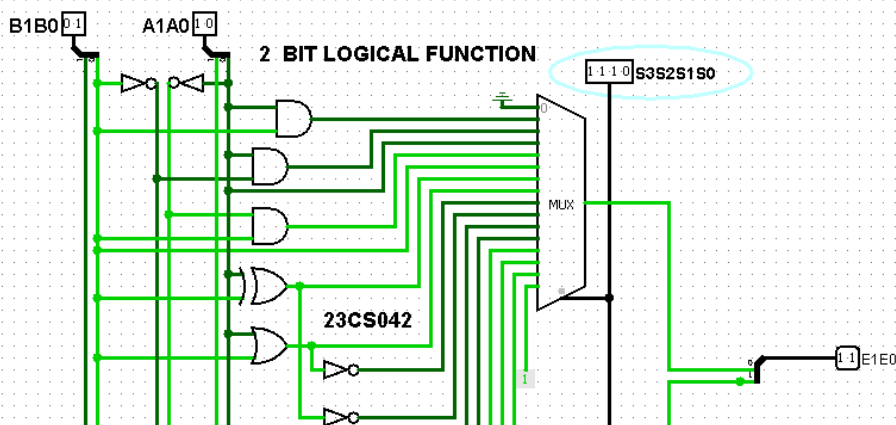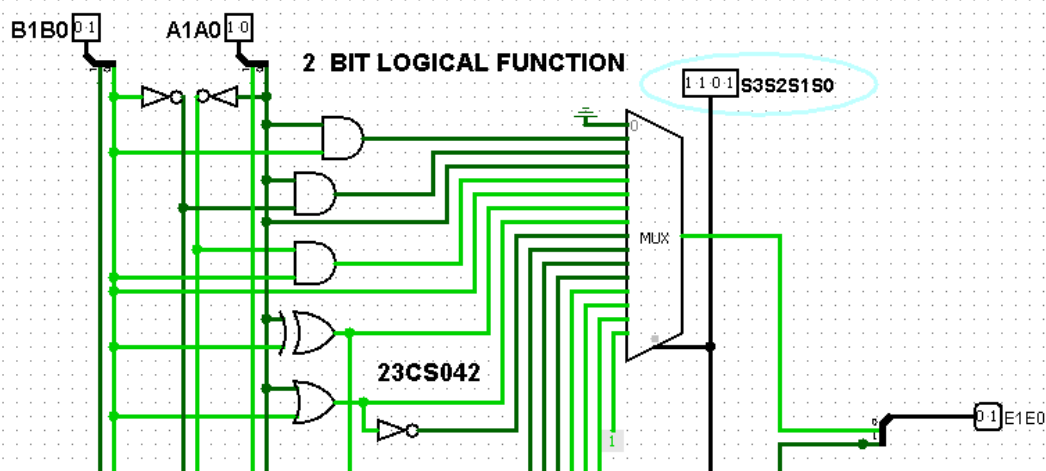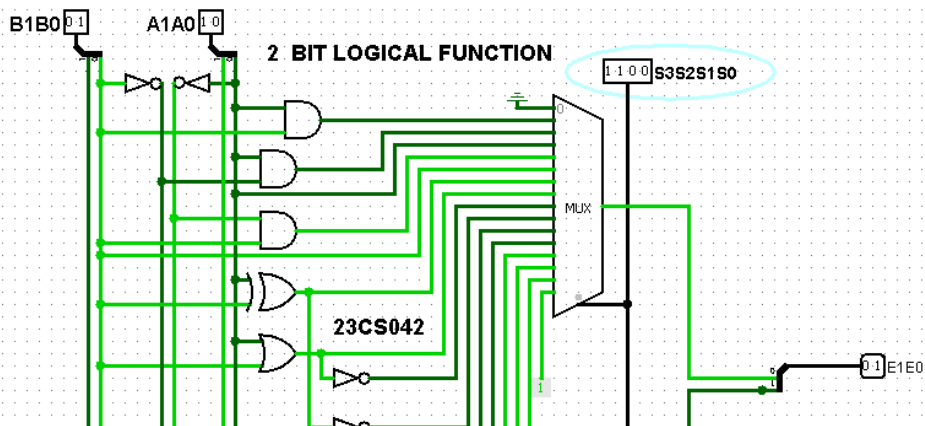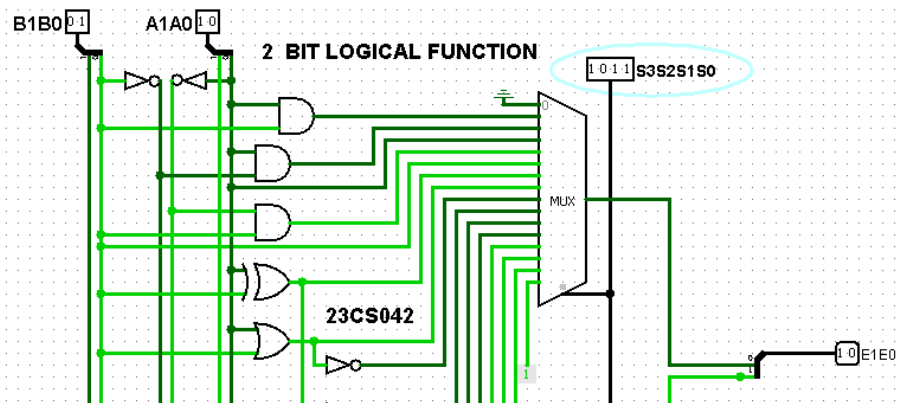


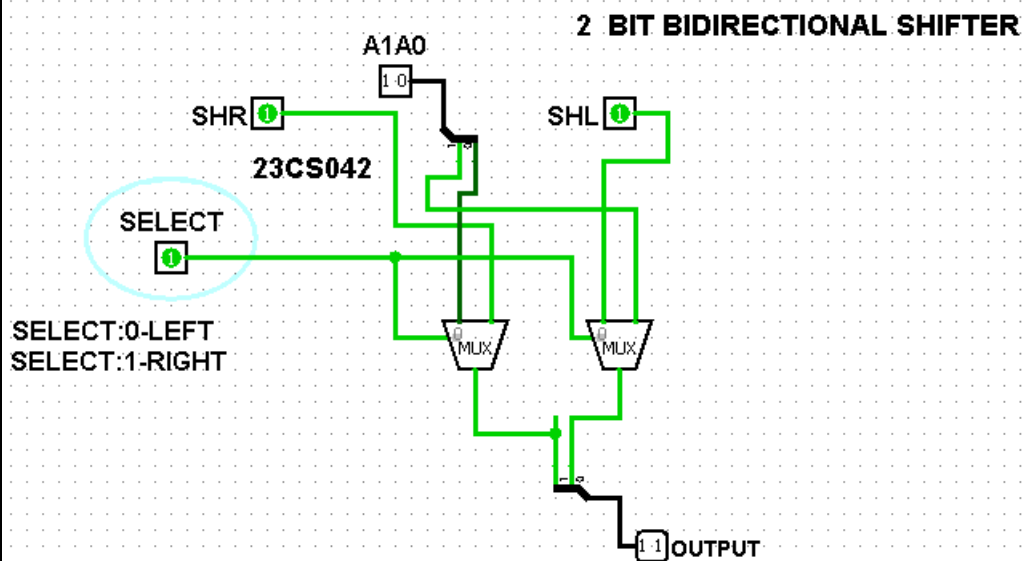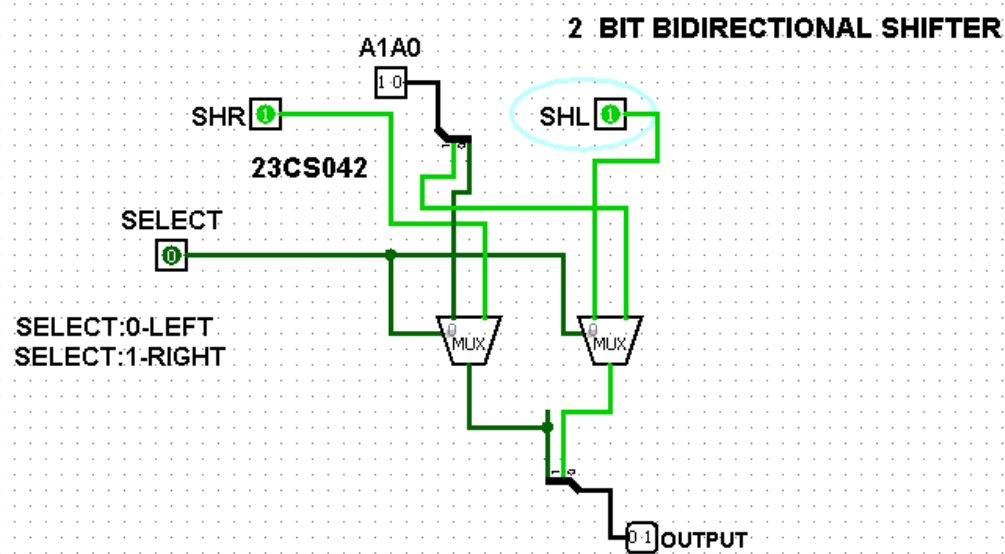
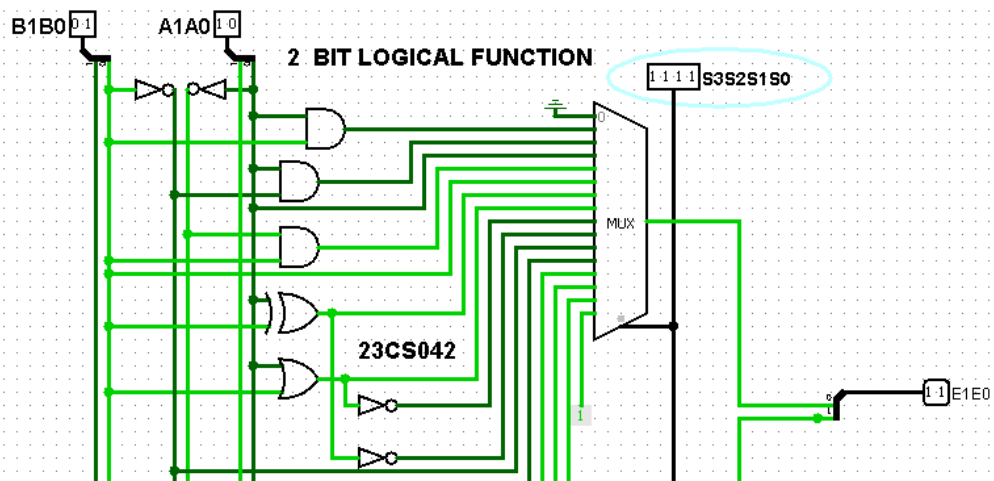




4 BIT BIDIRECTIONAL SHIFTER

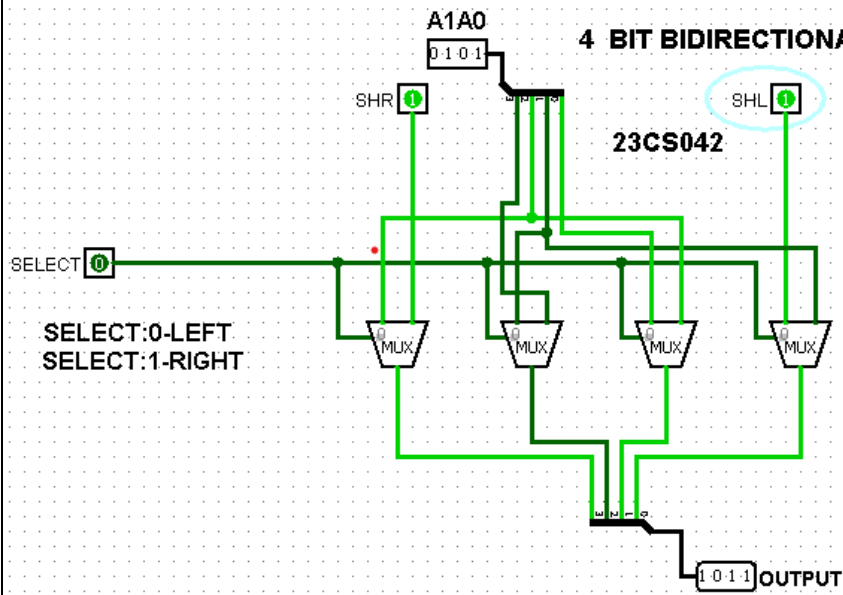



4 BIT BIDIRECTIONAL SHIFTER


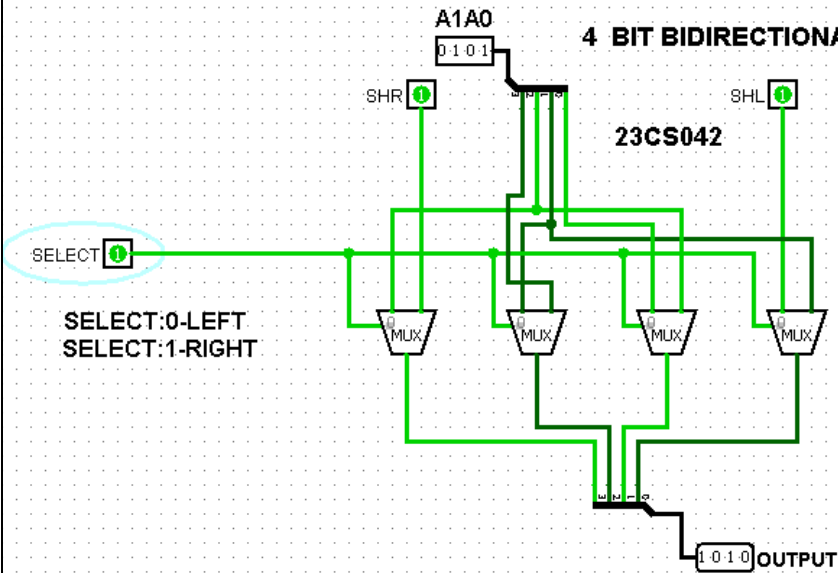


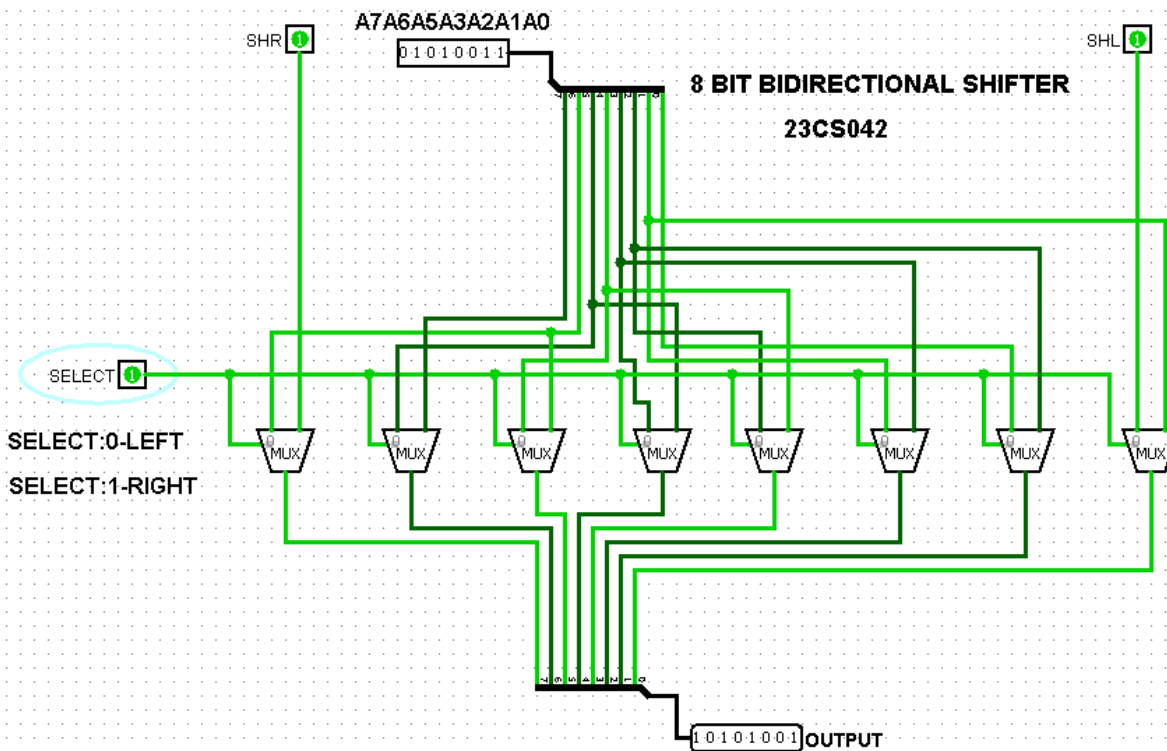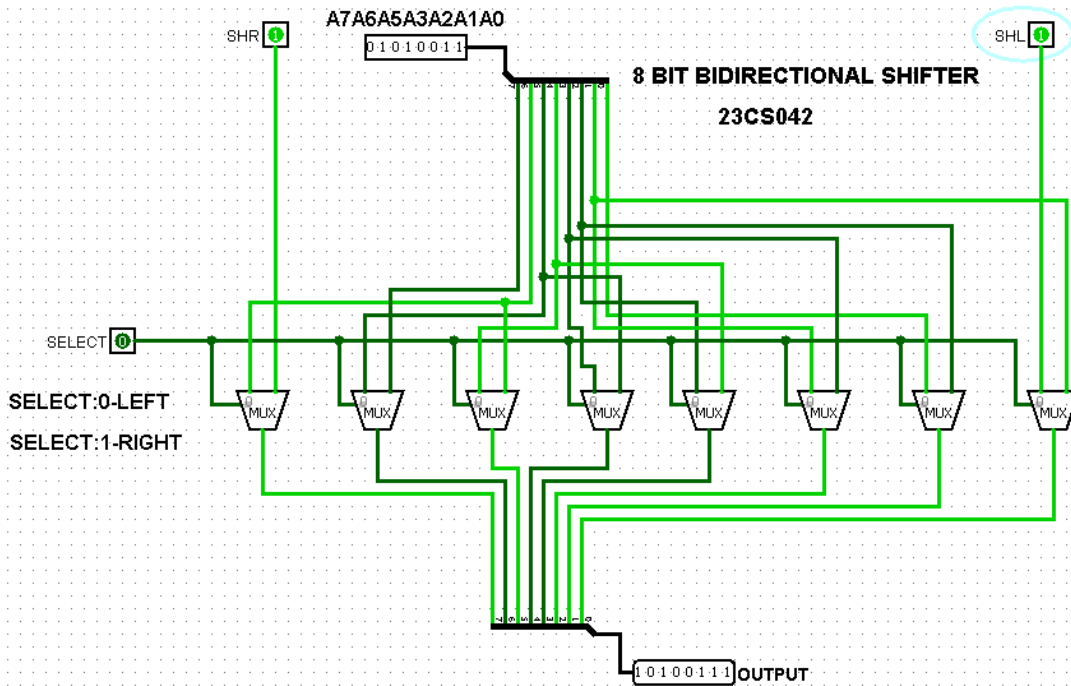


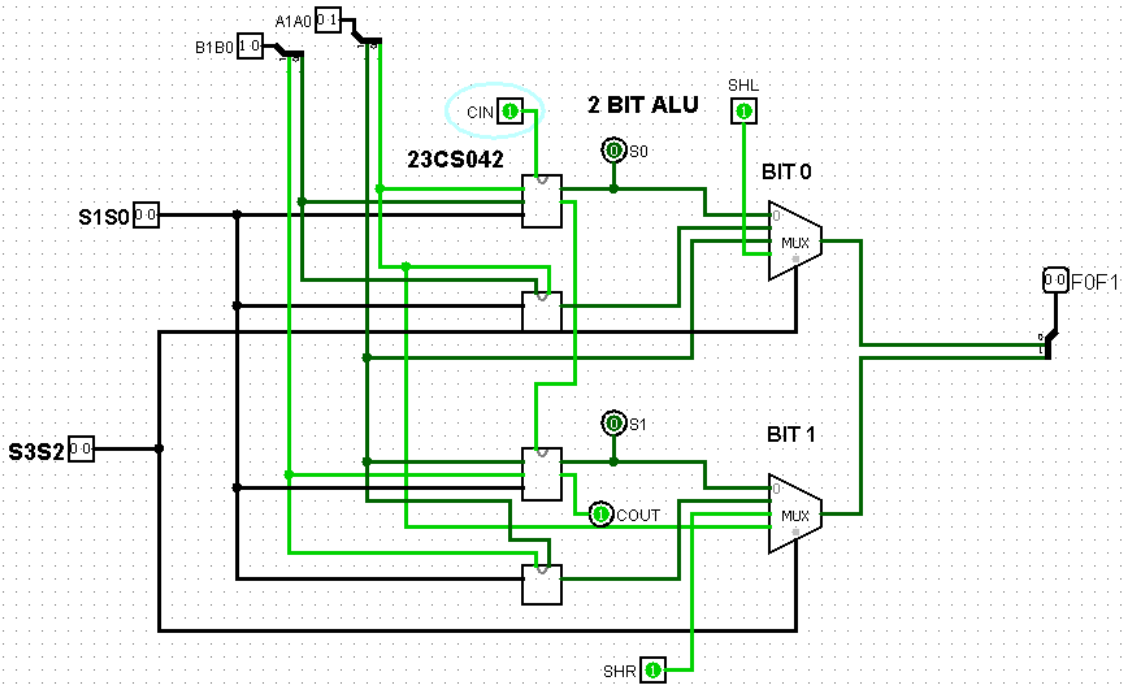
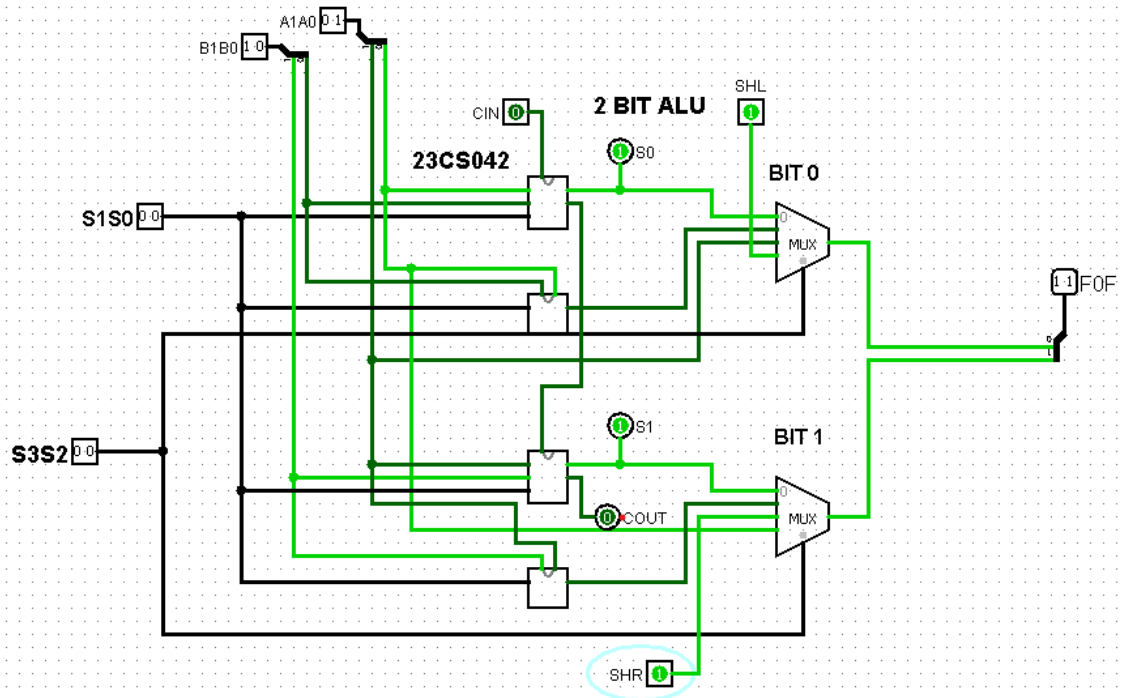


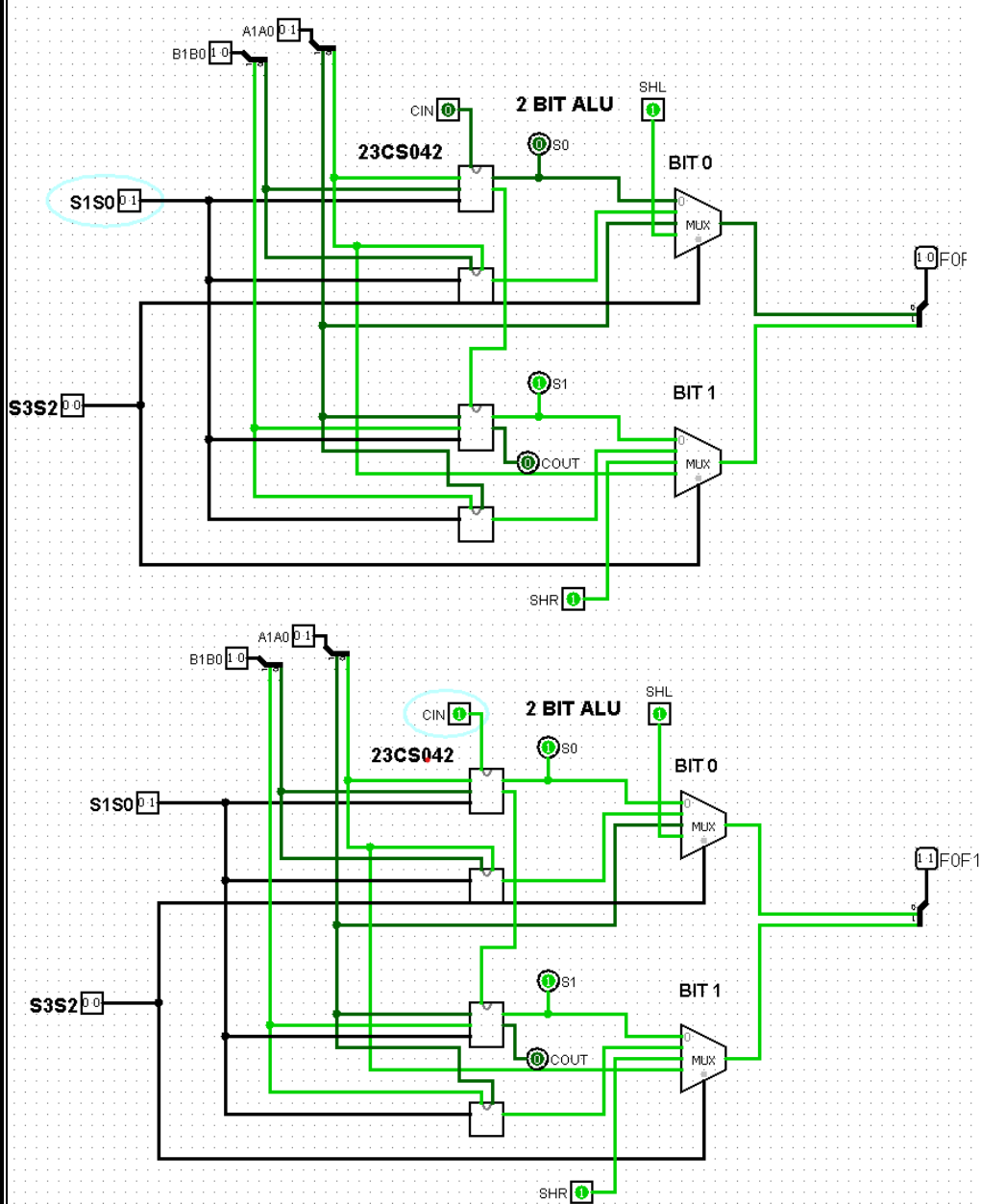


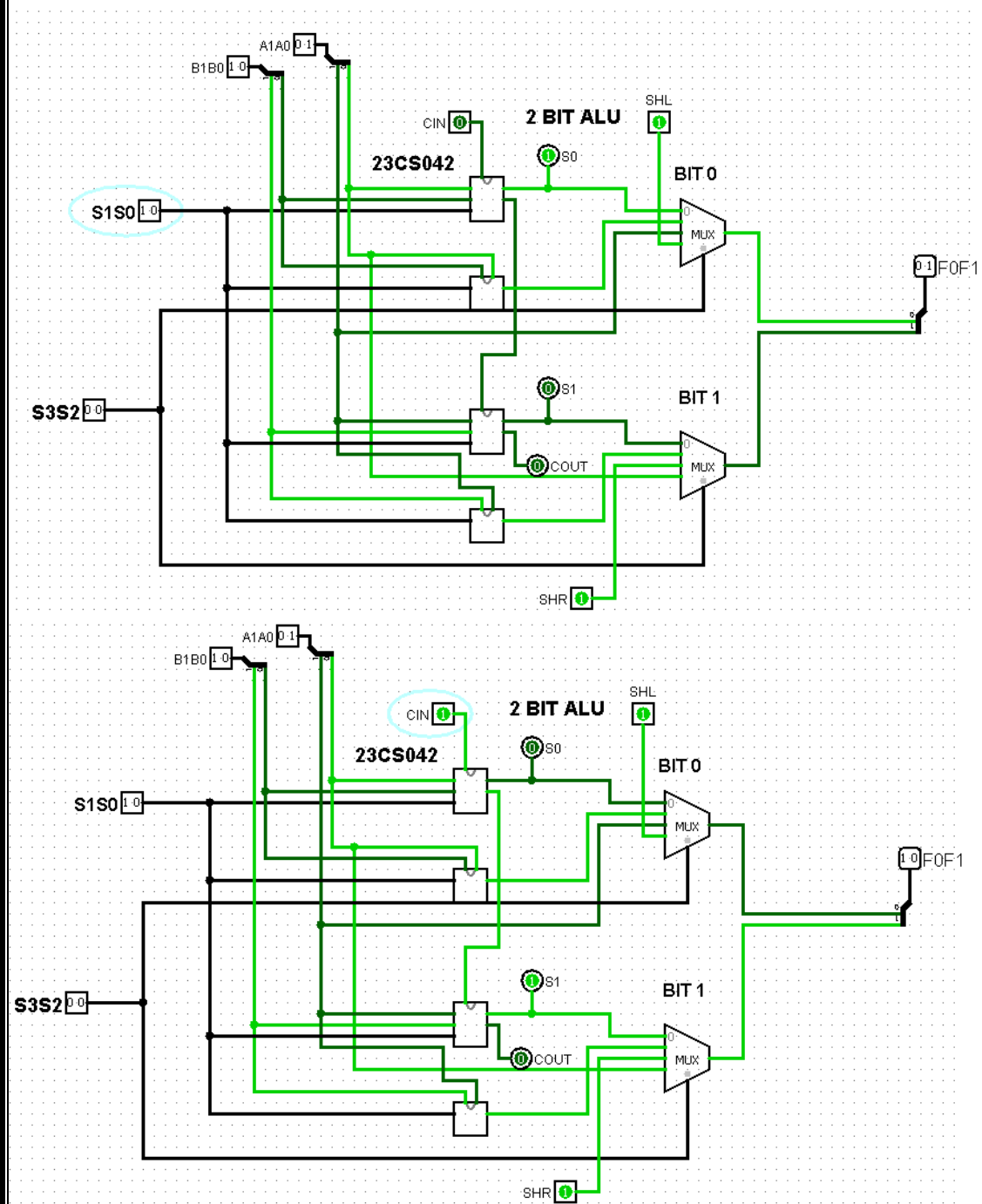


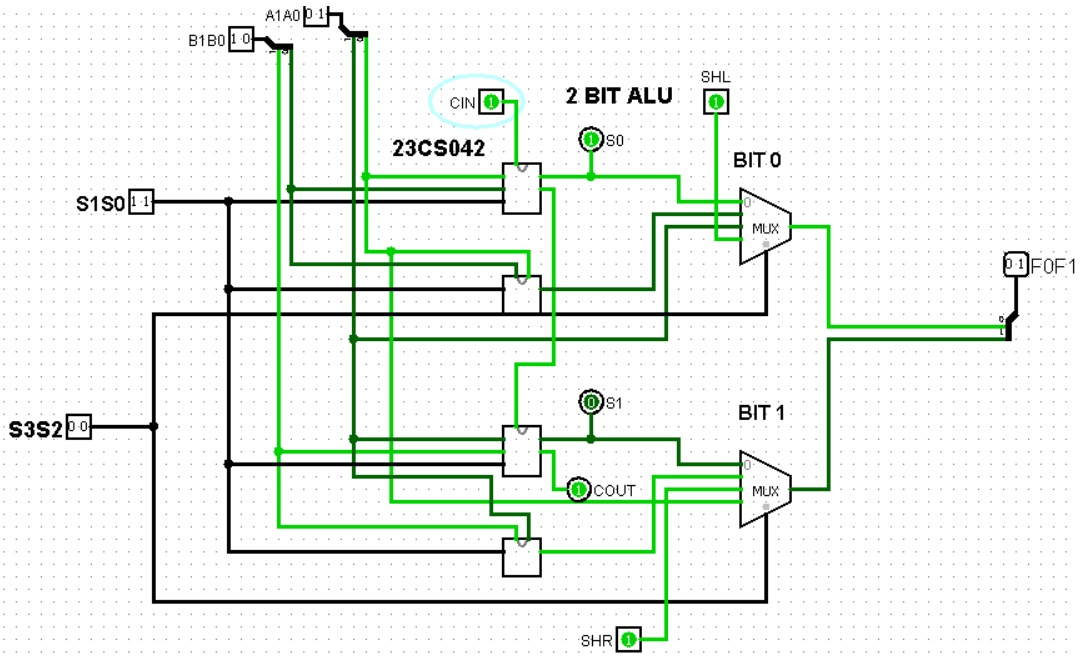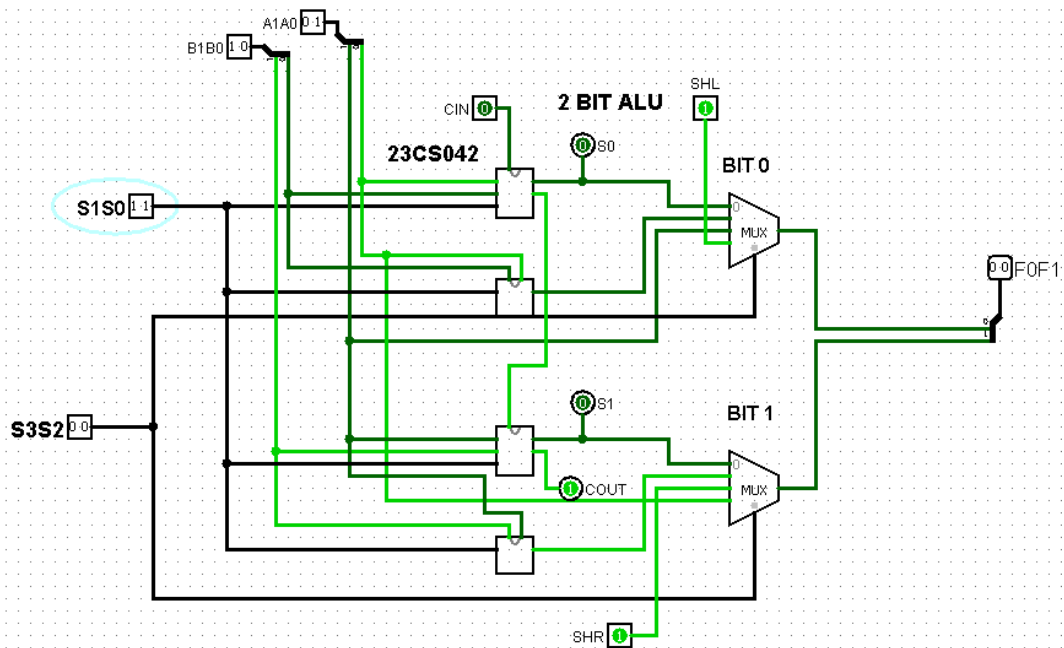


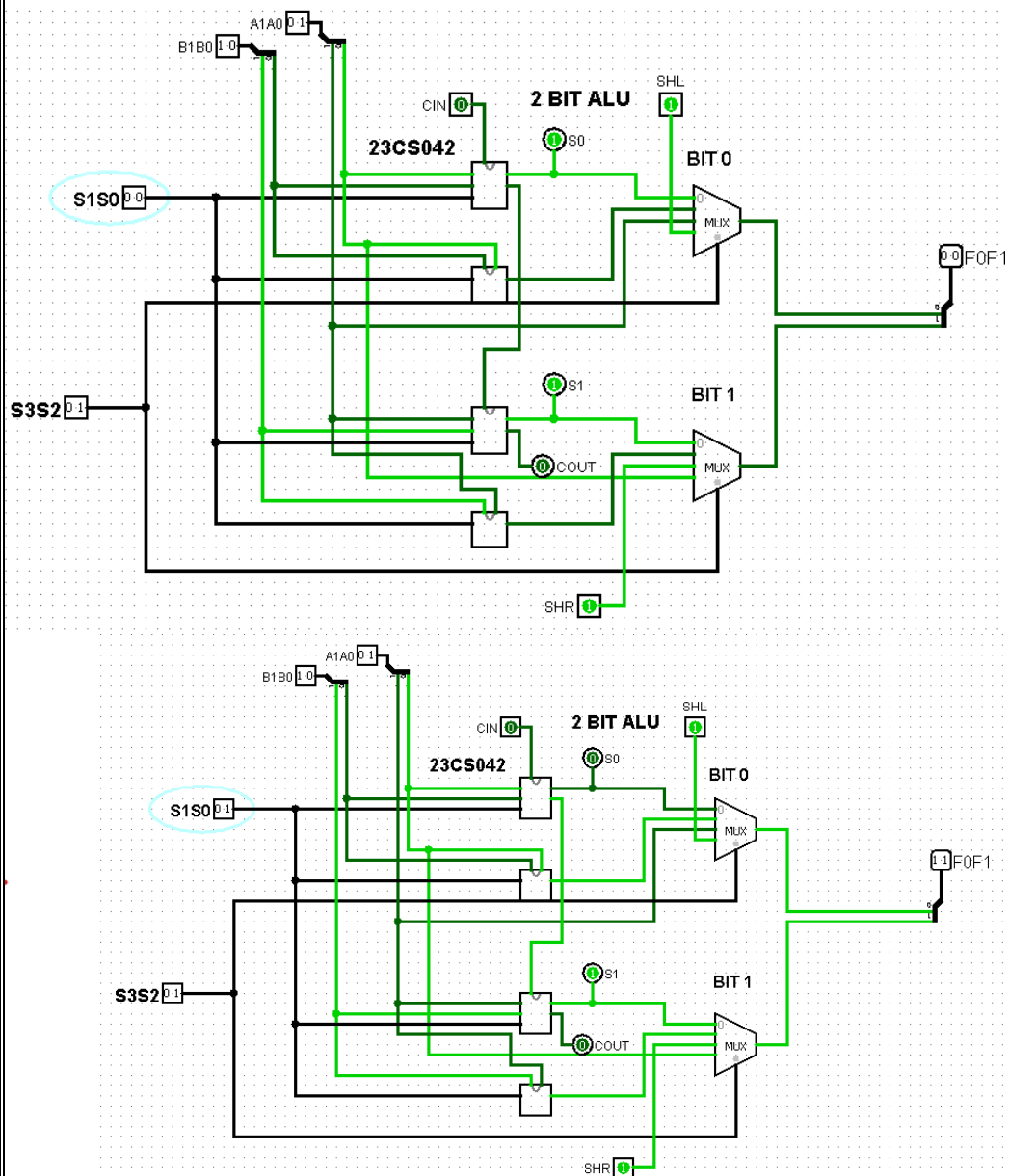

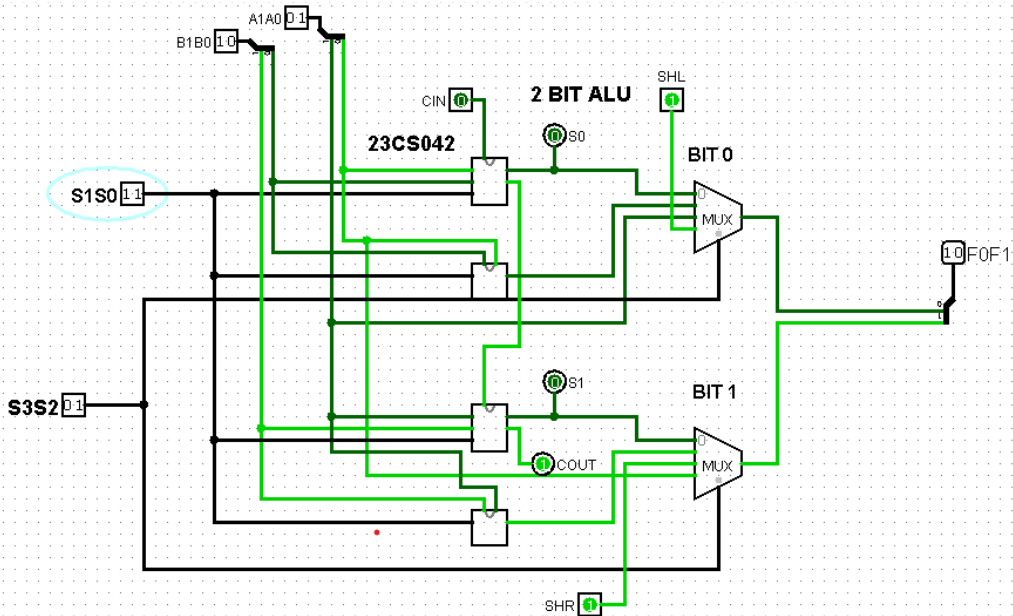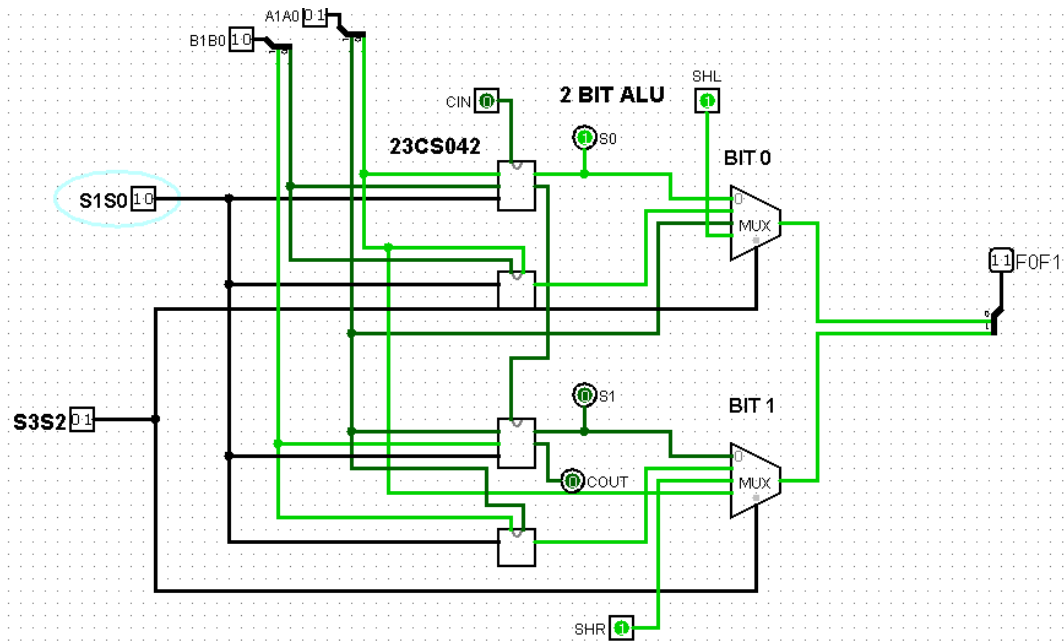

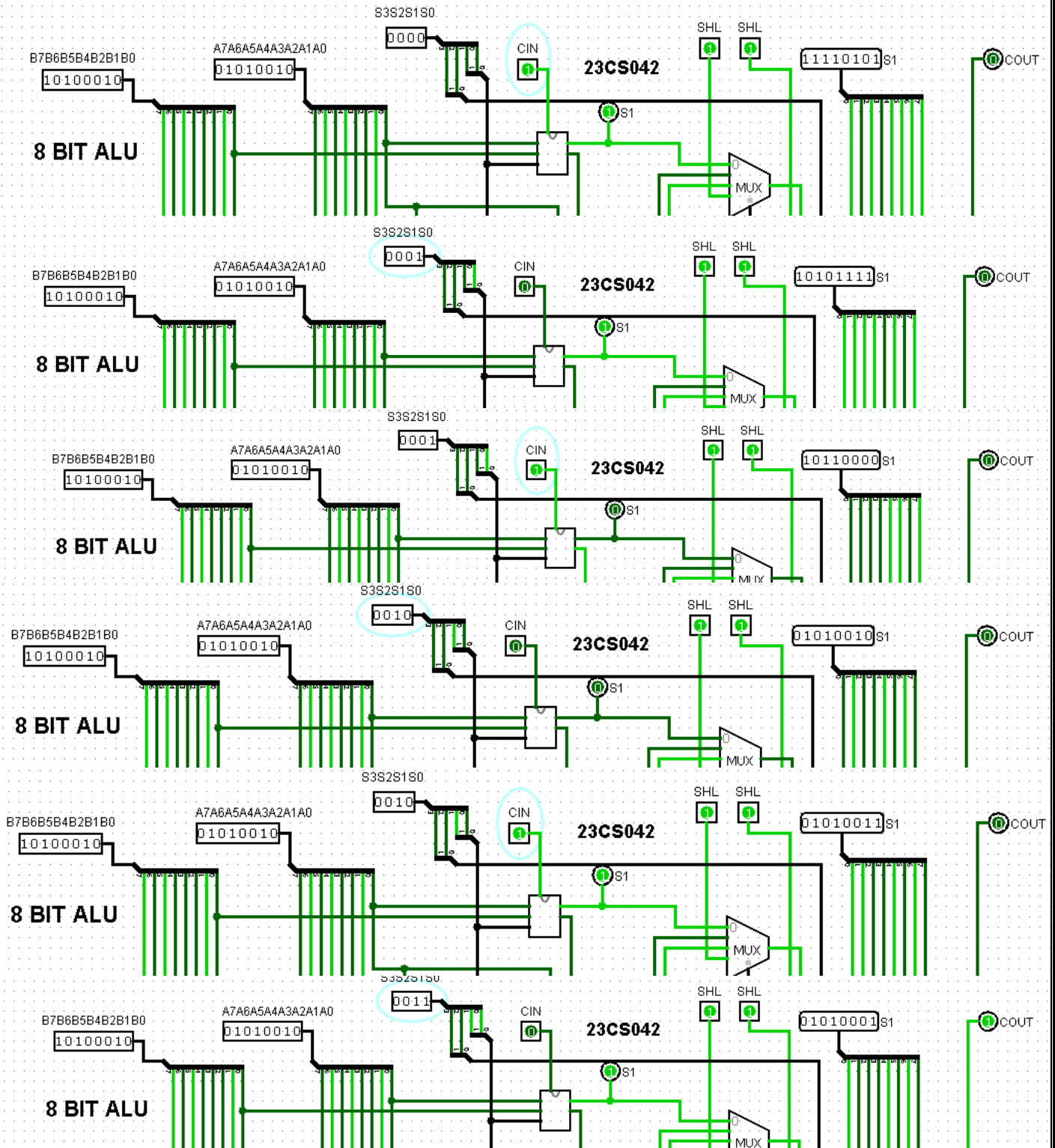

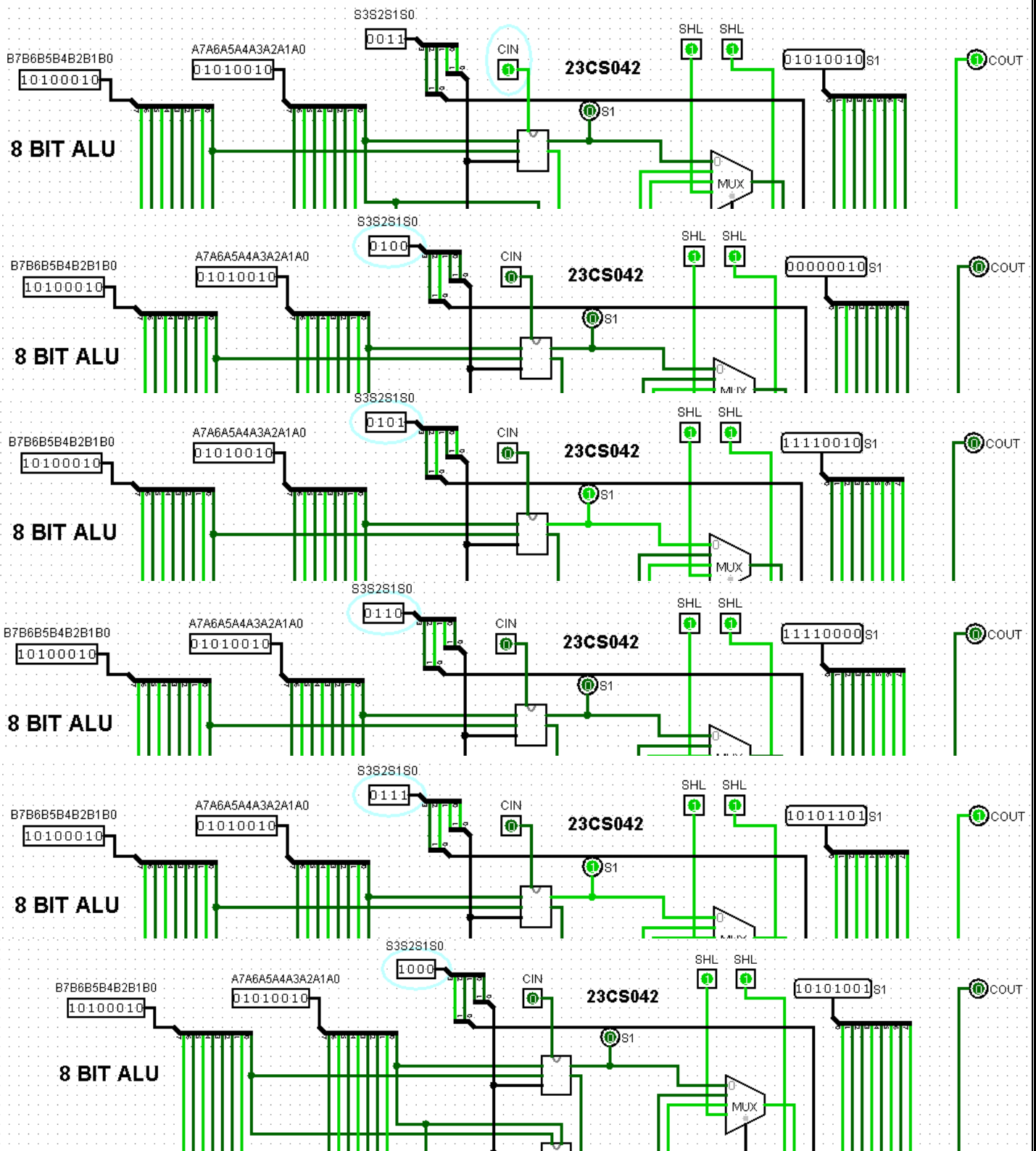

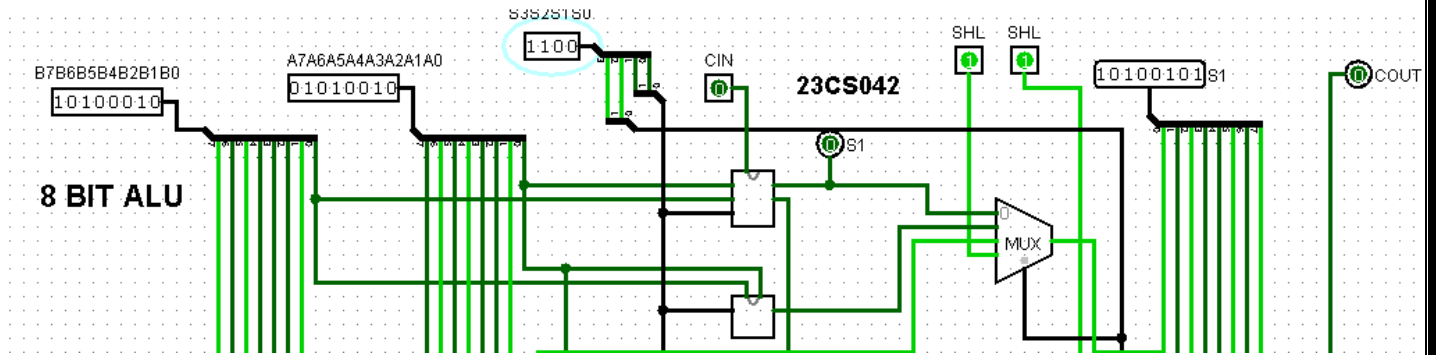

CONCLUSION: