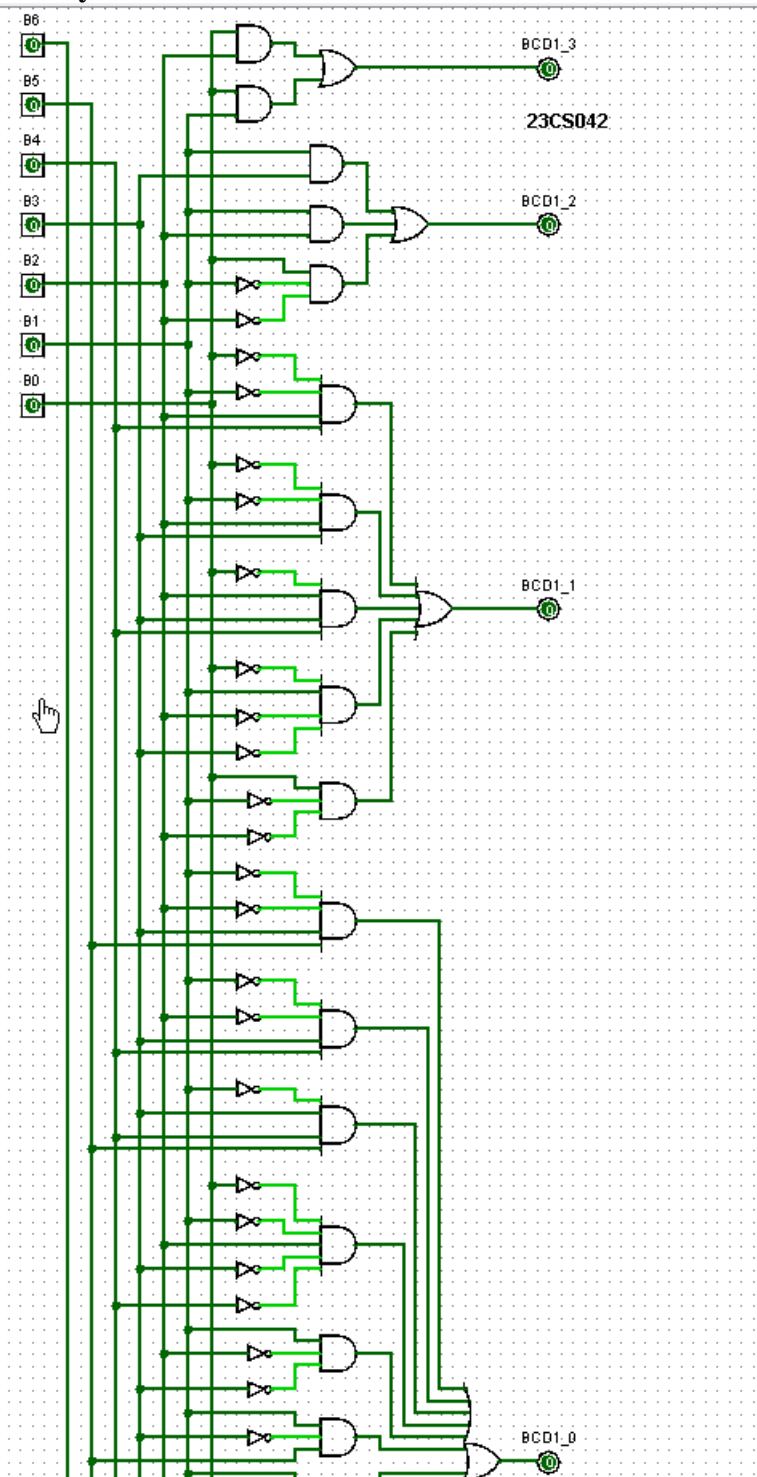



EXPERIMENT NO. 1


TASK: i. display 0 to 9 on a seven segment display with binary number as input
ii. display 0 to 99 using two seven segment displays with binary number as input


i. **display 0 to 9 on a seven segment display with binary number as input**



[illegible][illegible]





CIRCUITS:
Binary To Bcd

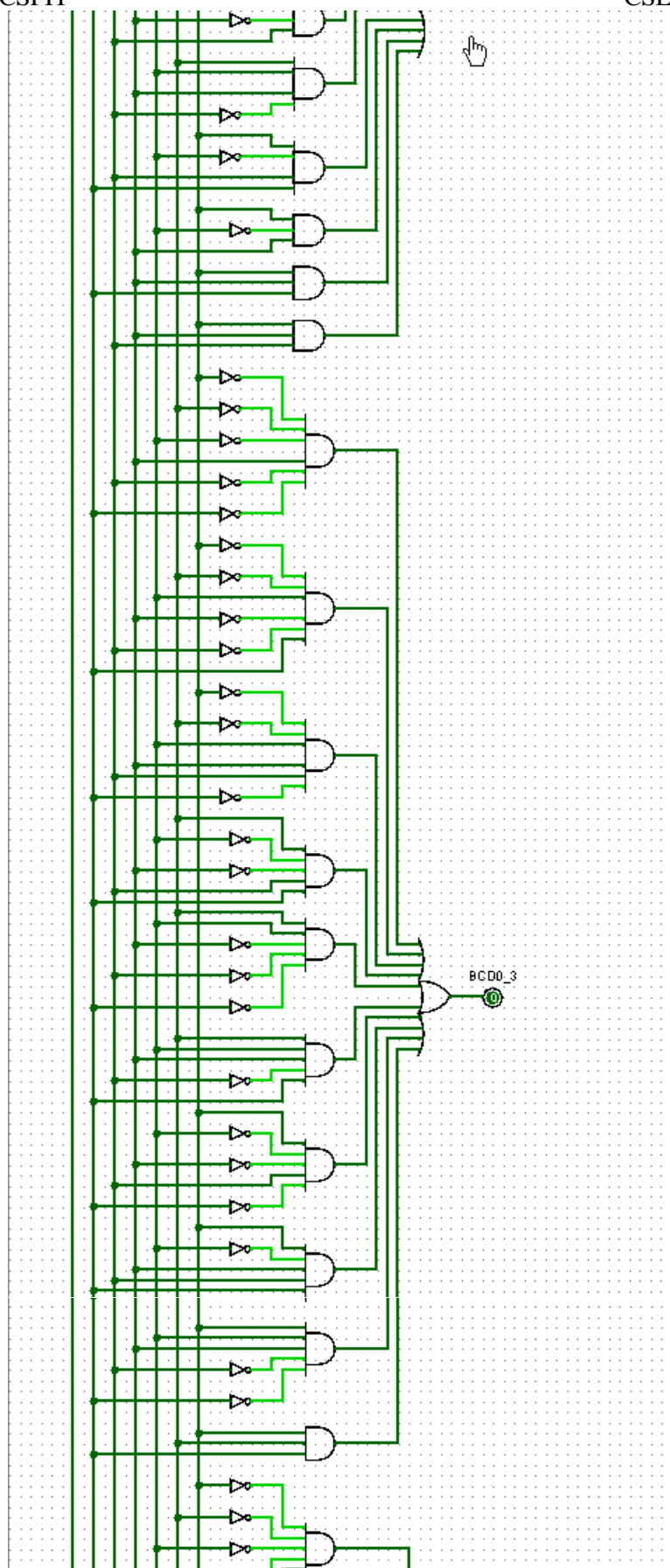


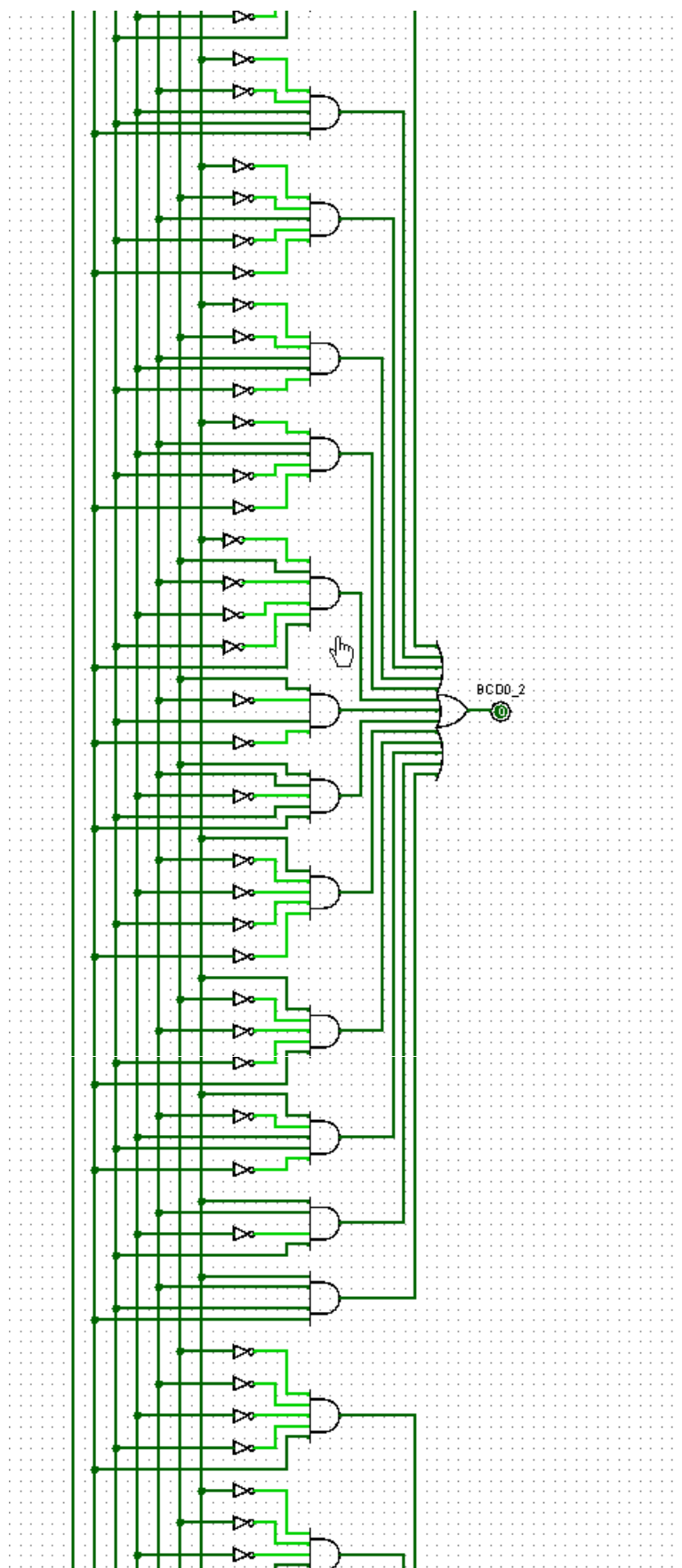

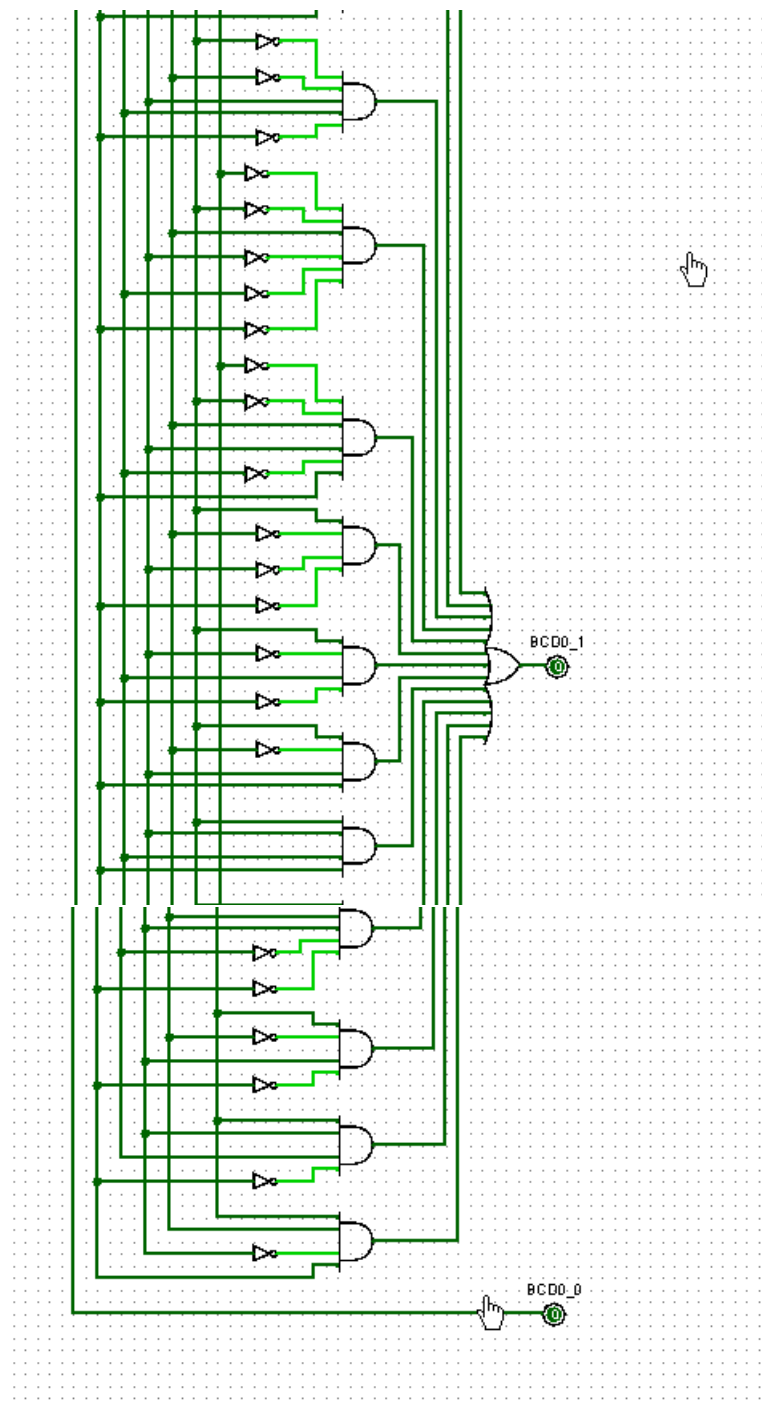

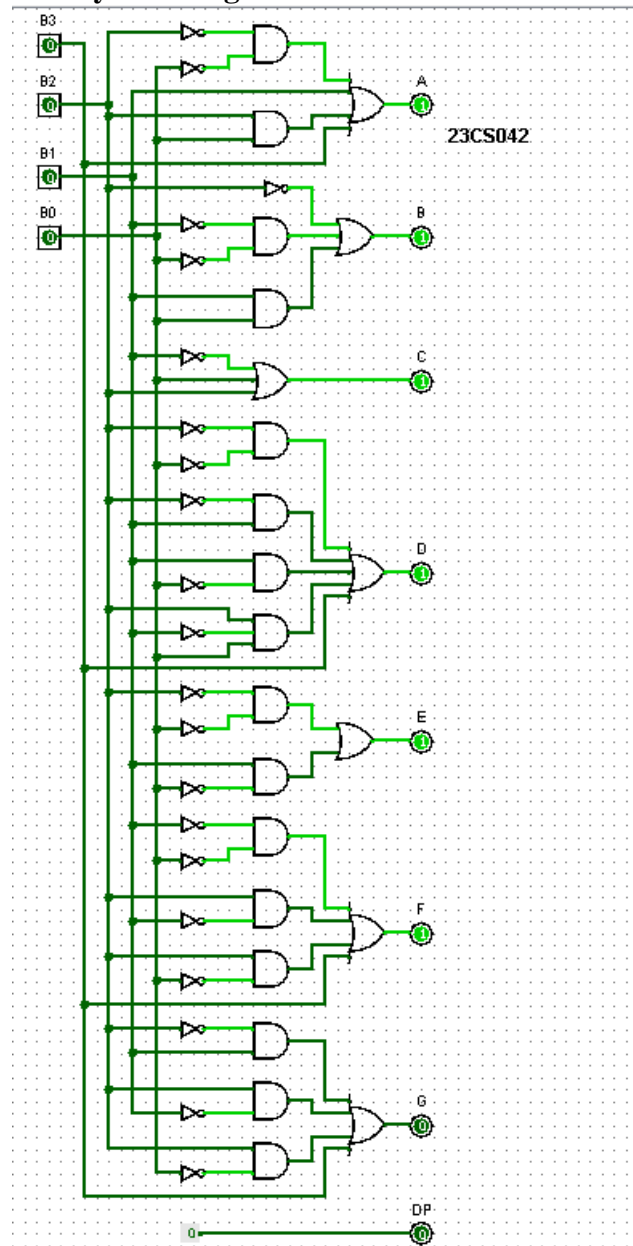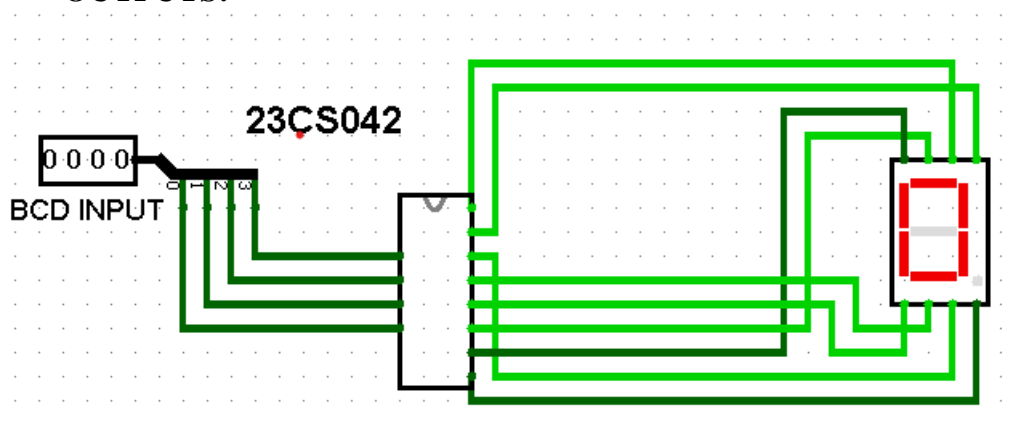Binary To 7 Segment**OUTPUTS:**

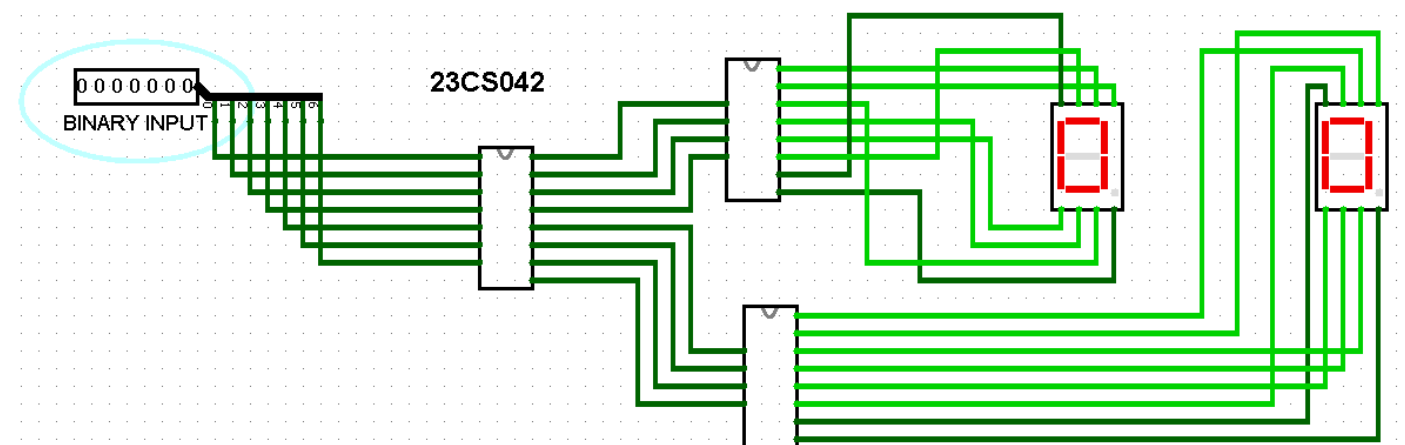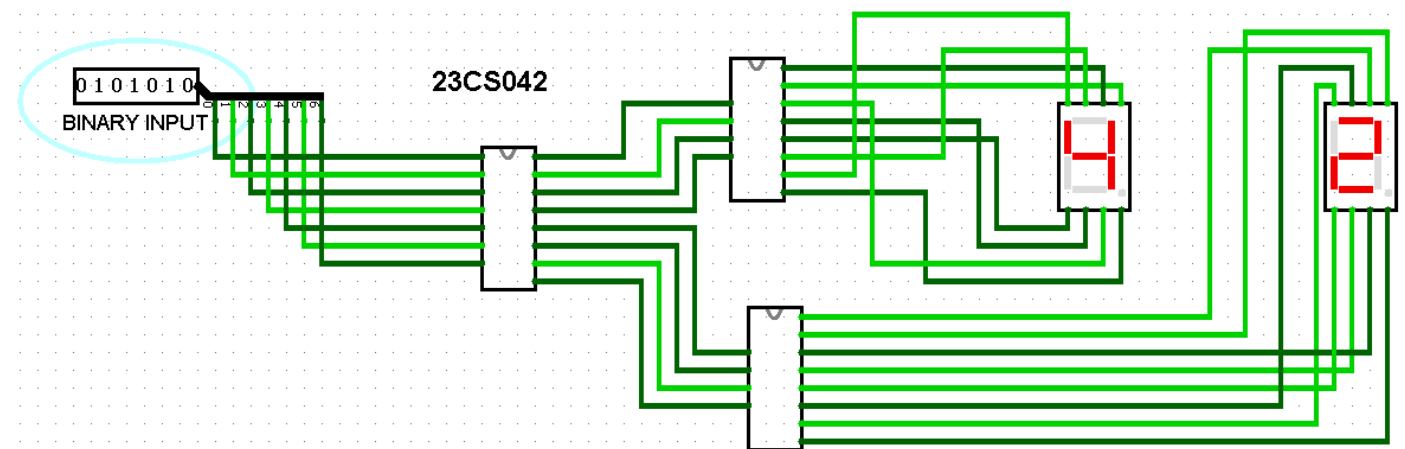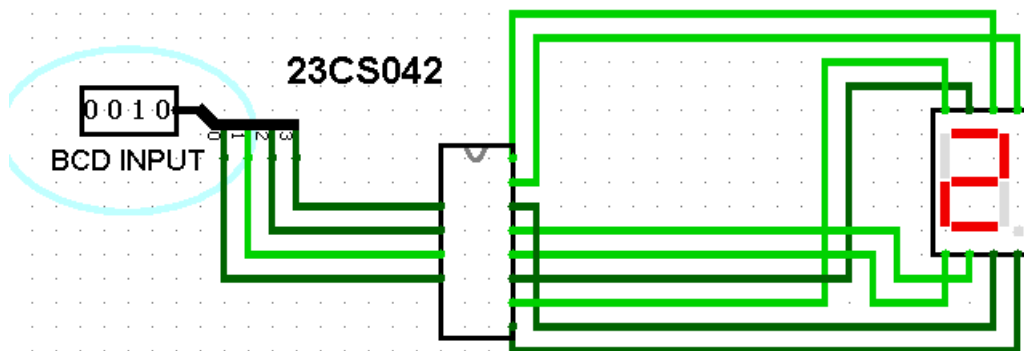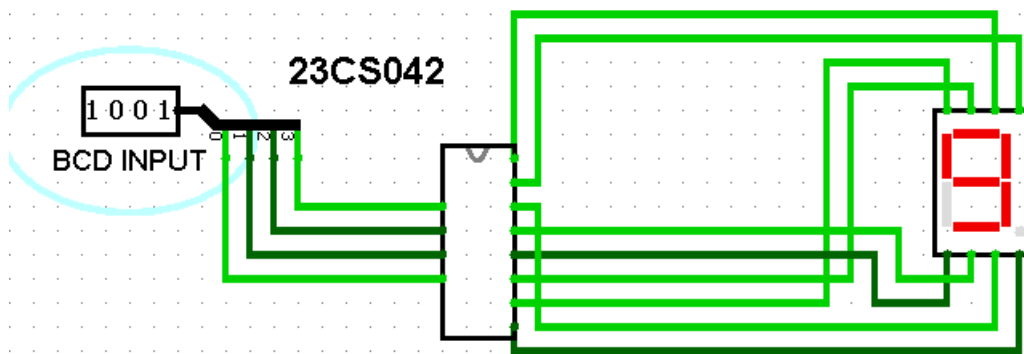

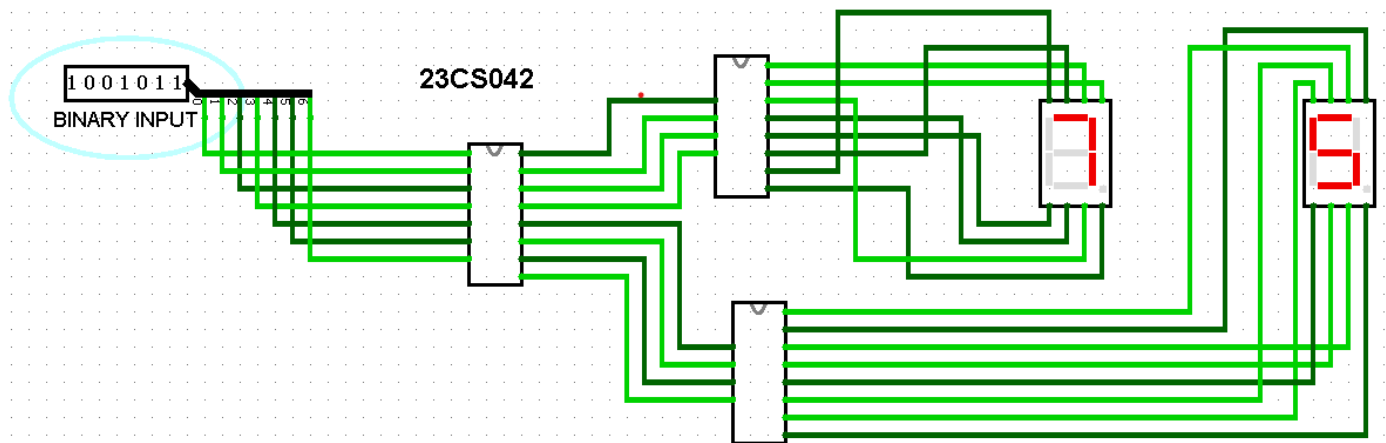

CONCLUSION: